

Practical No. 8: Demonstration of working of pulse transformer by observing input pulse and output pulse of pulse transformer on CRO.

I Practical Significance:

Pulse transformers can be divided into two major types, power type and signal type. The power type pulse transformer applications include precise control of heating elements fed from fixed DC source. The signal type pulse transformer delivers a pulse like signal or a series of pulses for temperature control. The turns ratio of the pulse transformer can be used to adjust signal amplitude and provide impedance matching between the source and load. Pulse transformers are often used in the transmittal of signal and in the gate drive circuitry of transistors, FETs, SCRs etc. Pulse transformer is a very essential and widely used device for low power circuits, high power switched mode power supplies and gate drive generation. Signal type of pulse transformers handle relatively low levels of power. The transformers are usually operated at high frequencies.

II Industry/Employer Expected Outcome(s)

Use Pulse Transformer to test its operation.

III Course Level Learning Outcome(s)

Select the Transformer and DC motor for the given application.

IV Laboratory Learning Outcome(s)

LLO Identify pin configuration of pulse transformer.

LLO Check electrical isolation between input and output of pulse transformer.


V Relevant Affective Domain related outcome(s)

Follow safety electrical rules for safe practices.

VI Relevant Theoretical Background

Pulse transformers are a diverse family of transformers designed to transfer a digital control signal from a control circuit to a load. They provide galvanic isolation to a circuit, whilst allowing fast control signal to be transmitted without distorting the signal shape. The input and output signal is typically a rectangular wave of a few volts with a frequency above 100kHz, not a sinusoidal wave as with conventional transformers. Pulse transformers have a low number of windings and low inter winding capacitance. As they operated with high frequency signals, the core material must be able to cope with repeated magnetization and demagnetization. The turn's ratio is typically 1:1 as their main purpose is to increase or transform the voltage, but to maintain it across the isolation barrier.

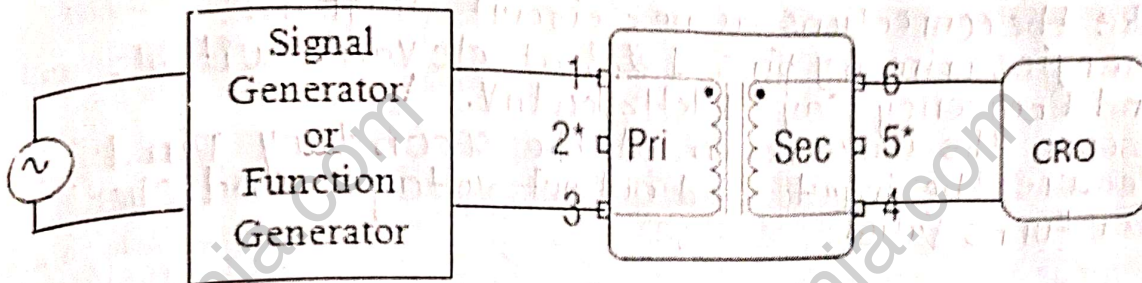VII Actual Circuit diagram used in laboratory with equipment Specifications:



VIII Required Resources/apparatus/equipment with specification:

S. No.	Name of Resource	Suggested Broad Specification	Quantity
1	Pulse transformer of suitable rating	Input voltage and frequency of relevant rating. 1 vpp signal at 1kHz	1
2	CRO	10 Hz- 30 MHz	1
3	Function generator	0.1 Hz - 11 MHz	1

IX Precautions to be followed:

1. Follow safety practices.
2. Do not make any connections with the power supply is ON.

X Procedure

1. Make the connections as per circuit diagram.
2. Energies primary pins 1 & 3 at relevant suitable voltage and frequency say 1kHz, 100mV.
3. Observe the waveform at the secondary pin 4 & 6.
4. Measure the input and output voltage and check for turns ratio

XI Required Resources/apparatus/equipment with specification:

S. No.	Name of Resource	Suggested Broad Specification	Quantity
1	Pulse transformer of suitable rating	Input Voltage and Frequency of relevant range.	1
2	CRO	10Hz - 30 MHz	1
3	function generator	0.1Hz - 11MHz	1

XII Actual Procedure followed:

1. Make the connections as per circuit diagram.
2. Energise primary pins 1 & 3 at selected suitable voltage and frequency say 1 kHz, 100 mV.
3. Observe the waveform at the secondary pin 4 & 6.
4. Measure the input and output voltage and check for turns ratio.

XIII Observations:

Sr. No.	Input voltage(volt)	Output voltage (volt)	Nature of input waveform	Nature of output waveform
1	Pulse transformer of suitable ratio	1V	Square pulse	Square pulse
2	200 mV	2V	Square pulse	Square pulse
3	300 mV	3V	Square pulse	Square pulse
4	400 mV	3V	Square pulse	Square pulse

XIV Results:

The output voltage of the pulse transformer increase proportionally with the input voltage.

XV Interpretation of results:

The input voltage applied to the primary winding of the pulse transformer is stepped up at the secondary voltage.

XVI Conclusion and recommendation:

The pulse transformer successfully demonstrated its function by accurately transferring the input pulse to the output.

XVII Practical related questions (Provide space for answers)

1. Why the pulse transformer has less number of turns and low inter winding capacitance.
2. Compare between conventional transformer and pulse transformer.
3. List applications of pulse transformer.

1. Pulse transformers have turns to reduce inductance and allow the transfer of high-frequency signals without distortion. low inter-winding capacitance minimize capacitive coupling, ensuring clean pulse transfer and voltage waveform distortion.

Feature	Conventional Transformer	pulse transformer
Application	Power transmission	Signal and pulse transfer
frequency range	low-freq	high-frequency pulses
Turns	Typically higher	Relatively lower
Core material	Laminated iron core	Ferrite or air core
Inter-winding capacitance	higher	lower

3. • switching power supplies
• pulse generation circuits
• communication equipment
• Radar and telecommunication systems
• Isolation between control and power circuits

XVIII References/Suggestions for further reading:

1. www.electrical4u.com
2. www.howstuffworks.com
3. www.electricaltechnology.org