
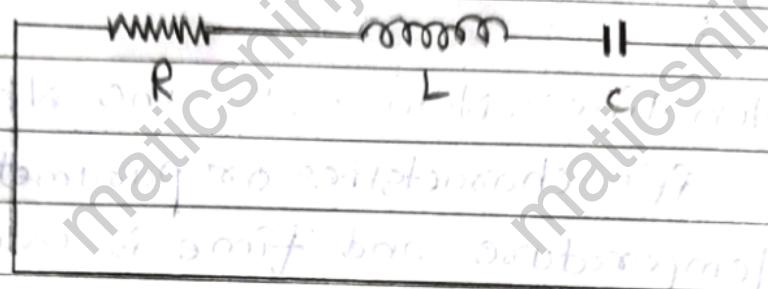


Unit 1 Single Phase A.C. Series Circuits

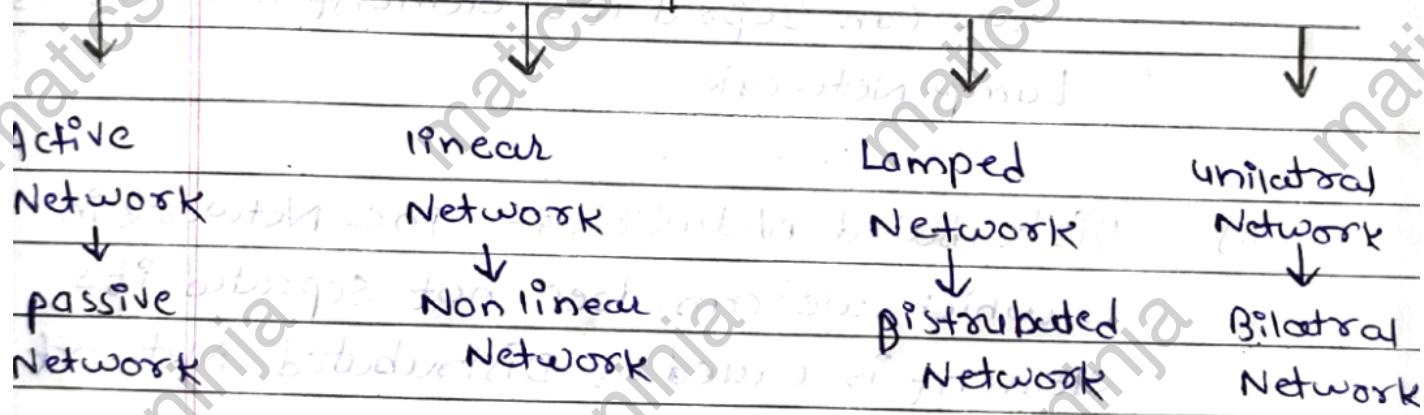Network :- All active elements or passive element when are electrically connected to each other it forms a network.



Network



1) **Active Network :-** The Network which contains any energy source or active element is called as Active element or Network.

2) **Passive Network :-** The Network which does not contain any energy source or passive element is called as passive Network.

3) Linear Network & The Network in which it's characteristics or parameters does not change with time and temperature is called as linear Network.

4) Non-linear Network & The Network in which it's characteristics or parameter changes it's temperature and time is called as Nonlinear Network.

5) Lumped Network & The Network in which we can separate it's element is called as Lumped Network.

6) Distributed Network & The Network in which we can not separate it's element is called as Distributed Network

7) Unilateral Network & The Network in which it's characteristics does not change with change in direction of current is called as unilateral Network.

8) Bilateral Network & The Network in which it's characteristics change with change in direction of current is called as Bilateral Network.

★ Circuit Element :-

1) Resistor :-

It is a material which oppose the flow of current through it.

Resistance :- It is the property of material which opposes the flow of current through it.

$$R = \rho \frac{l}{a}$$

$$\rho \propto l = H.M$$

It's unit is Ω

$$R = \text{---} \quad \text{fixed Resistor}$$

$$R = \text{---} \quad \text{Variable Resistor}$$

* Inductor :-

Inductor is a material which opposes change in current through it.

Symbol for inductor

$$L = \frac{N \times \phi}{I} \quad \text{Value is given by } L$$

It's unit is Henry

it also measured in

$$\text{mH} = 10 \times 10^{-3}$$

$$\mu\text{H} = 1 \times 10^{-6}$$

$$V = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int V dt$$

current through a inductor

* Capacitor :-

Capacitor is a electronic device which stores the electrical energy in the form of static charge.

Conducting plate

dielectric medium

It is denoted by C

and it's SI unit is Farad.

Capacitors :-

Is a ability of capacitor to stored the electrical charge
It's unit is farad

It is given by

$$C = \frac{Q}{V}$$


$$Q = CV$$



eqn for current = $i = \frac{dQ}{dt} = C \frac{dV}{dt}$

eqn for voltage = $V = C \frac{dU}{dt}$




$$V = \frac{1}{n} \int i dt$$

* Simple Loop A.C Circuit.

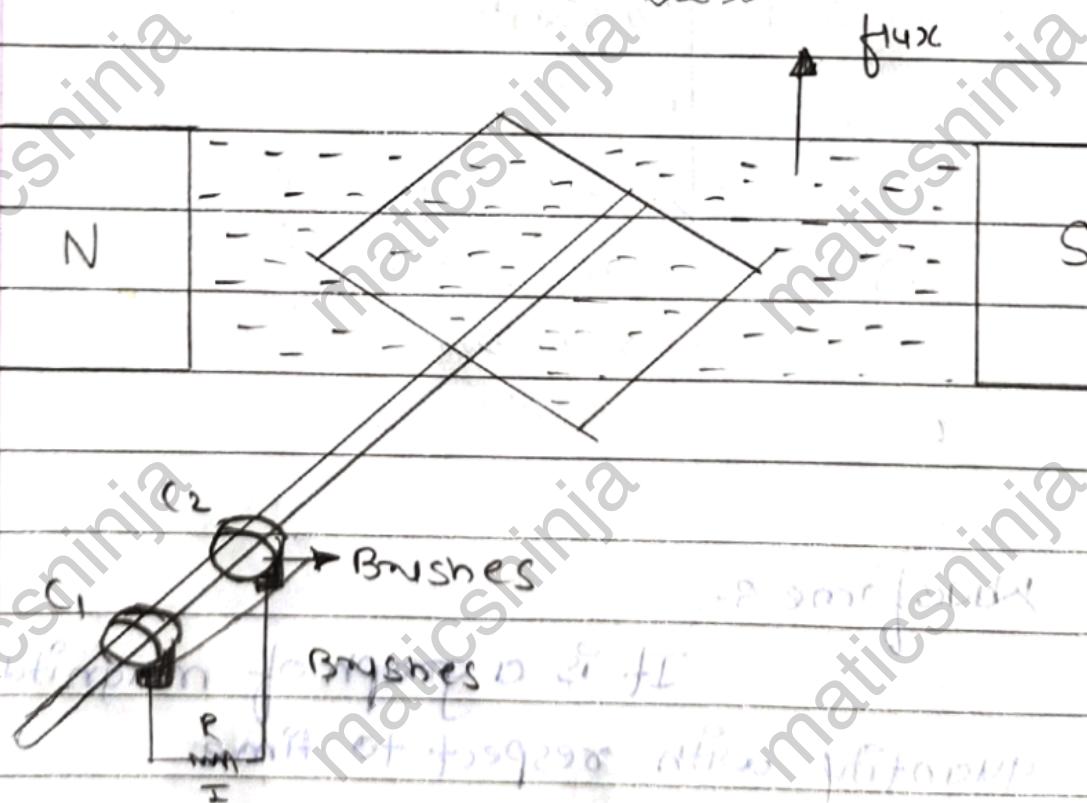

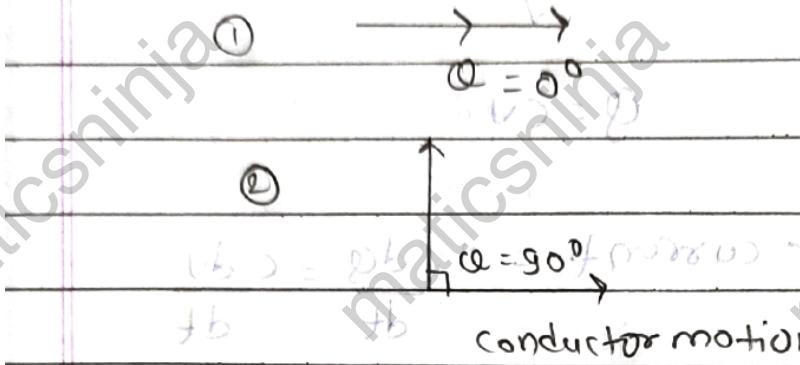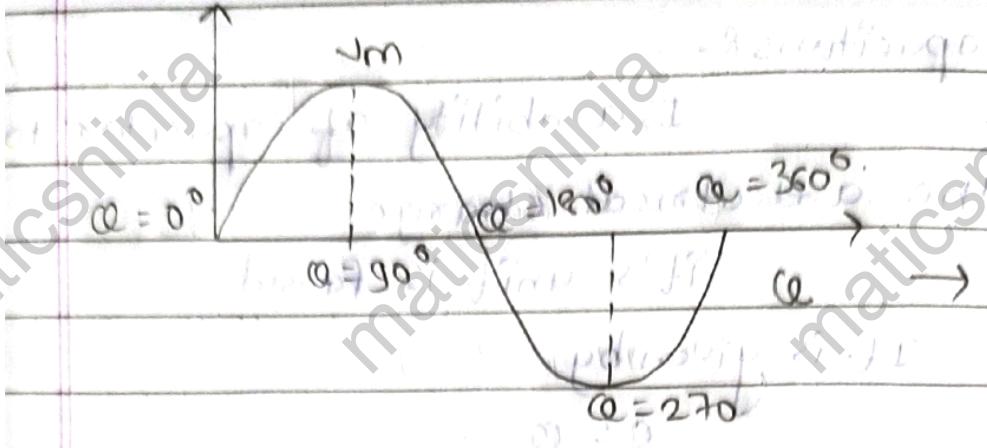

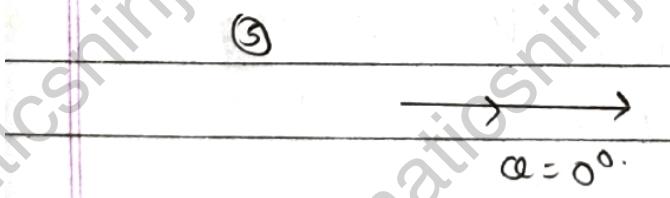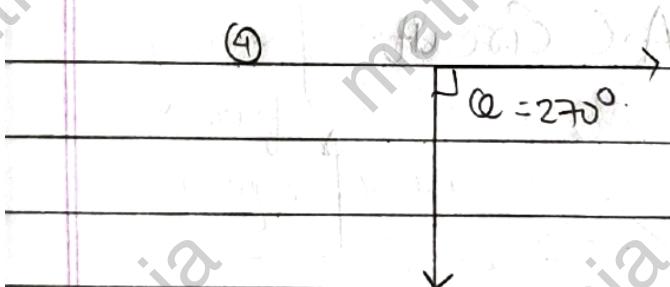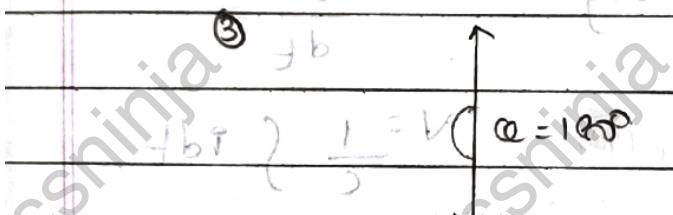$v_b \omega = f = \text{frequency of aps}$



1) Waveform &

It is a graph of magnitude of AC quantity with respect to time

2) Instantaneous value &

It is the value of AC quanti

at particular instant

3) Amplitude and peak value :-

It is a maximum value

of peak value of AC quantity

4) Cycle :-

Complete set of one positive half cycle
and one negative half cycle

5) Frequency :- The Number of cycles per second is
frequency (Hz)

6) Time period :- Time required to complete one
cycle is time period

RMS Value :-

RMS value or effective value

is equal to Stady stat current or DC current
which produce same amount of heat as produced
by AC current with temperature and resistance
Remains constant

$$\text{RMS value} = 0.707 \text{ Vm}$$

$$\text{or } \frac{\text{Vm}}{\sqrt{2}}$$

Average value :-

It is a average of all instantaneous
value taken over a one half cycle

$$\text{VAV} = 0.637 \text{ Vm}$$

g) Peak factor or Crest factor &

It is the ratio of peak value and Rms value is a peak factor

Peak value

Rms value

$$= \frac{\text{Peak value}}{\text{Rms value}}$$

$$= \frac{\text{Peak value}}{\sqrt{\text{RMS}}}$$

$$= \frac{\text{Peak value}}{(SH) 0.707 \sqrt{\text{RMS}}}$$

$$= 1.414$$

ii) Form factor &

It is a Ratio of Rms value to

average value

Rms value

Average value

Rms

Ave

$$= 0.707 \sqrt{\text{RMS}}$$

$$= 0.637 \sqrt{\text{RMS}}$$

Directly proportional to

$$\text{Step down ratio} = 1.109$$

$$= 1.109 \times 0.637 \sqrt{\text{RMS}}$$

→ What is the Average value of sinusoidal Alternating current of 31 A maximum value.


Given, $I_m = 31 \text{ A}$.

$$I_{\text{Avg}} = 0.637 \times I_m$$
$$= 0.637 \times 31$$

$$I_{\text{Avg}} = 19.74 \text{ A}$$

$$I_{\text{RMS}} = 0.707 \times I_m$$
$$= 0.707 \times 31$$
$$= 21.91 \text{ A}$$

* Phase Representation :

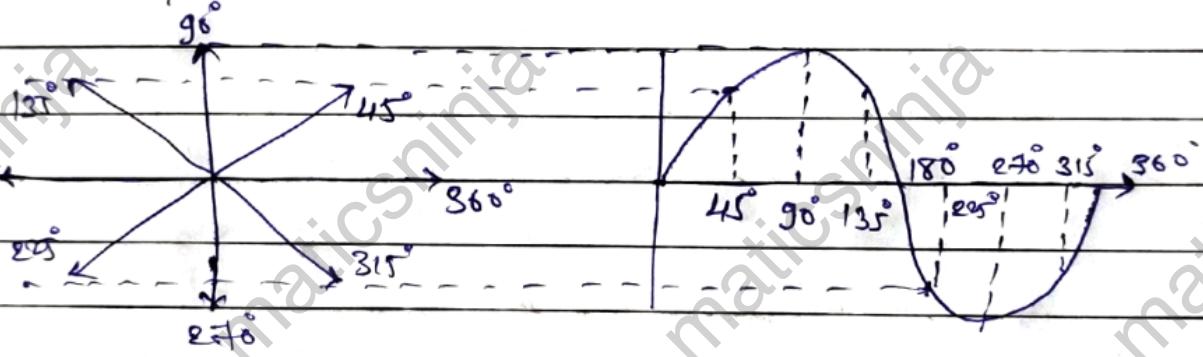

- It is a straight line with an arrow mark on one side. The length of this straight line represents the magnitude of the sinusoidal quantity & the arrow represents its direction.

* Phasor Representation of an Alternating Quantity

① Phase Angle (θ) :

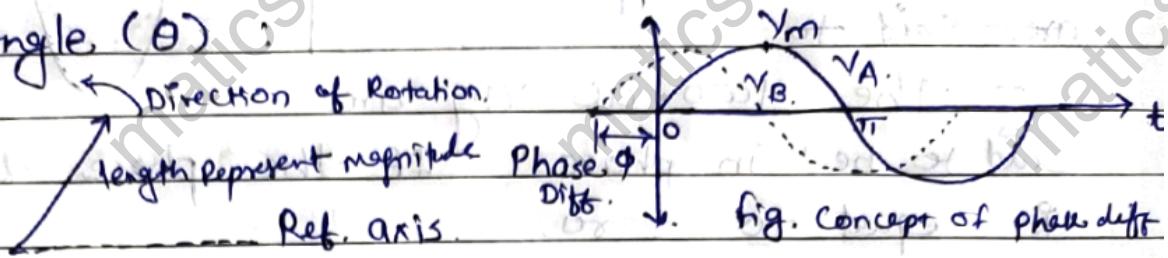


fig. Concept of phase diff.

- The angle, made by the conductor w.r.t. the magnitude Reference axis, is called as phase angle

② Phase Difference : The phase diff. is the difference in the phase angle of two AC Sinusoidal AC waveform.

- The angle ϕ is known as the Phase difference betn V_A & V_B . It is measured in 'Radians'.

Types of Phase difference :

- ① Leading Phase diff. ② Lagging Phase diff.
- ③ In phase diff.

① Leading Phase diff. :-

If the phase angle ϕ is positive then the phase diff. ϕ is said to be a leading phase diff. In other words we say that V_B leads V_A .

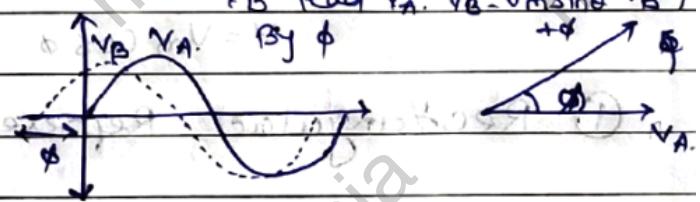


fig. Concept of leading phase diff.

② Lagging Phase diff. :-

If the phase angle ϕ is negative then the phase diff. ϕ is said to be a lagging phase diff. In other words we say that V_B lags V_A .

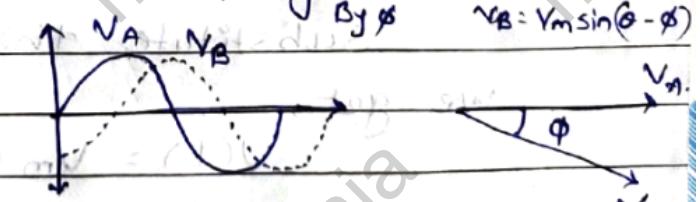



fig. Concept of lagging phase diff.

③ If phase diff. is

- The two v_{tg} V_A & V_B are said to be

- The two ac v_{tg} are

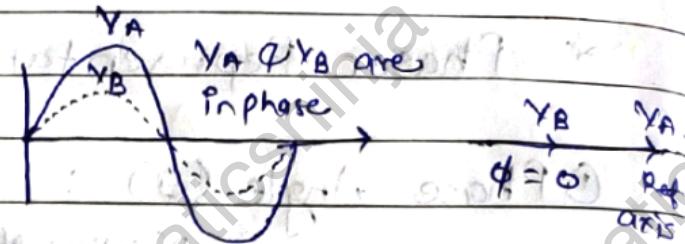said to be "in phase." If the phase diff. bet' them is equal to zero.




Single Phase AC Circuit

= Mathematical Representation of Phasor:-

- A phasor can be presented in two diff. ways:

① Rectangular form

② Polar form

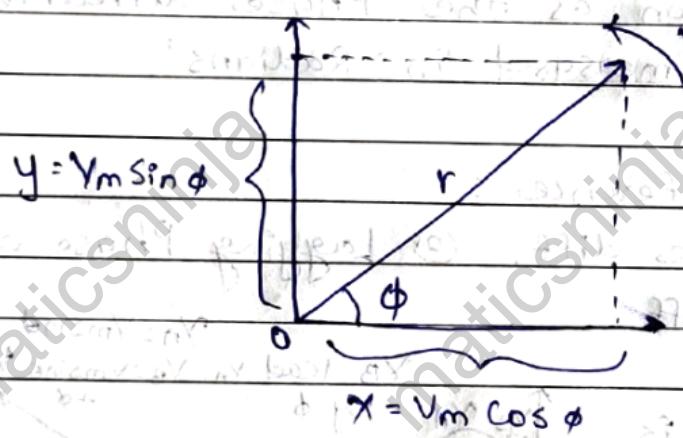

① Rectangular Representation

$$V(t) = x + jy \quad \text{--- (1)}$$

x = x Component of the phasor = V_m cos φ

y = y Component of the phasor = V_m sin φ

Substitute the value of x & y in eqn (1)
we get,

$$V(t) = V_m \cos \phi + j V_m \sin \phi$$

e.g. If $V(t) = 20 \sin(100\pi t + 60^\circ)$ can be represent in the rectangular form as follow

$$\begin{aligned} V(t) &= (20 \cos 60^\circ + j 20 \sin 60^\circ) \\ &= 10 + j 17.32 \end{aligned}$$

② Polar Representation

- the instantaneous v(t) = $V_m \sin(\omega t + \phi)$ can be represented in the polar as follow:

$$v(t) = r \angle \phi$$

where $r = V_m$

e.g. $v(t) = 20 \sin(100\pi t + 60^\circ)$ is represented in the polar form as,

$$v(t) = 20 \angle 60^\circ \text{ volt.}$$

* Conversion from polar to Rectangular :

$$v(t) = r \angle \phi \quad |z| = r \cos \phi, y = r \sin \phi.$$

$$v(t) = r \cos \phi + r \sin \phi$$

e.g. $z = 10 \angle 60^\circ$ ~~$\therefore z^2 = 100$~~

$$z = 10 \cos 60^\circ + j 10 \sin 60^\circ$$

$$\therefore z = 5 + j 8.66$$

* Conversion from Rectangular to Polar :

$$v = x + jy \quad r = \sqrt{x^2 + y^2}, \theta = \tan^{-1} \left(\frac{y}{x} \right)$$

$$r = \sqrt{x^2 + y^2} \quad \& \quad \theta = \tan^{-1} \left(\frac{y}{x} \right)$$

e.g. $16 + j8$

$$r = \sqrt{(16)^2 + (8)^2}$$

$$r = \sqrt{17.88} \quad | \quad \theta = 26.56$$

$$\boxed{17.88 / 26.56}$$

e.g. or Numerical

1) Convert $z = 6 + j8$ in polar form

Soln: $z = 6 + j8$ in Rectangular form

$$\therefore x = 6, y = 8$$

$$r/z = \sqrt{x^2 + y^2} = \sqrt{6^2 + 8^2} = 10 \text{ via}$$

$$0 = \tan^{-1}(\frac{y}{x}) \quad \tan^{-1}(\frac{8}{6}) = 53.13^\circ$$

$$\therefore z = 10 \angle 53.13^\circ \quad \text{Polar form}$$

2) Convert $z = 16 + j8$ in Polar form $= 17.89 \angle 26.57^\circ$

3) Convert $z = 20 - j34.64$ in Polar form: $\underline{40 \angle -60^\circ}$

H.W. $z = 4 + j\sqrt{5}$ in Polar $= 6.40 \angle 51.31^\circ$

Rectangular $30 \angle 60^\circ$ in Rec. $= 15 + j25.98$

① Convert $z = 10 \angle 60^\circ$ in Rectangular form =

Soln: $z = 10 \angle 60^\circ$

$$= 10 \cos 60^\circ + j 10 \sin 60^\circ$$

$$z = 5 + j 8.66 \sqrt{2} \quad \text{Rectangular form}$$

② Convert $z = 18 \angle 30^\circ$ in Rect. form $= \underline{15.58 + j9}$

③ Convert $z = 20 \angle 60^\circ$ in Rec. form $= \underline{10 + j17.32}$

Addition & Subtraction by Using Rect. form

$$v_1 = x_1 + j y_1$$

$$v_2 = x_2 + j y_2$$

Add: $(v_1 + v_2) = (x_1 + x_2) + j (y_1 + y_2)$

Similarly

Sub: $(v_1 - v_2) = (x_1 - x_2) + j (y_1 - y_2)$

Multiplication & Division by using Polar form:

$$v_1 = r_1 \angle \phi_1$$

$$v_2 = r_2 \angle \phi_2$$

Multi. $(v_1 \cdot v_2) = (r_1 \cdot r_2) \angle \phi_1 + \phi_2$

Div of $\frac{v_1}{v_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$

Note : For Addition & Subtraction, represent the phasors in their rectangular form.
for Multiplication and Division represent the phasors in their Polar form.

* Single Phase AC Circuits

- The three Basic elements of any AC circuit are Resistance (R), Inductance (L) & Capacitance (C).
- We are going to discuss the following three ac circuit first and then their Combination.
- The three basic AC circuit are :
 - ① Purely Resistive AC circuit
 - ② Purely Inductive AC circuit
 - ③ Purely Capacitive AC circuit

To understand these AC circuit we should have the to understand Reactance & Impedance.

* Reactance and Impedance

In the circuit we have defined 'Resistance' as opposition to the flow of current. Similarly for a.c circuit we defined two terms namely 'Reactance' & Impedance (Z).

Reactance : Reactance can be of two types:
① Inductive Reactance (X_L)
② Capacitive Reactance. (X_C)

① Inductive Reactance (X_L):

Inductive Reactance is defined as the opposition to the flow of an alternating current offered by an inductance.

It is denoted by X_L & measured in (Ω)

$$X_L = \omega L$$

$$\therefore [X_L = 2\pi f L]$$

② Capacitive Reactance (X_C):

The Capacitive Reactance is defined as the opposition to flow of current offered by a pure capacitor.

It is denoted by X_C

The expression for capacitive reactance is,

$$X_C = \frac{1}{\omega C} \quad [X_C = \frac{1}{2\pi f C}]$$

③ Impedance (Z):

An Impedance is defined as the opposition offered by combined effect of resistance and reactance to the flow of alternating current.

It is denoted by Z

Impedance can be expressed in the Polar form as follows

$$Z = |Z| \angle \phi$$

where $|Z|$ = Magnitude of Z

ϕ = Phase Angle.

It is expressed in the Rectangular form as follows:

$$Z = R + jX$$

Where, R = Resistive Part

X = Reactive Part

Numerical :

- 1) Find out Resistance and Capacitance of the given impedance .
- 1) $25 \angle -45^\circ \Omega$
 - 2) $10 - j 15 \Omega$

Soln : 1) $10 - j 15 \Omega^2 = 25 \angle -45^\circ$

Convert polar to Rectangular

$$R = z \cos \phi = 25 \cos (-45^\circ) = 17.67 \Omega$$

$$X_C = j z \sin \phi = j 25 \sin (-45^\circ) = -17.67 \Omega$$

$$\therefore z = R - j X_C$$

$$z = 17.67 - j 17.67 \quad \text{--- Rect. form}$$

$$X_C = \frac{1}{2\pi f C} \quad C = \frac{1}{2\pi \times 50 \times 17.67}$$

$$X_C = \frac{1}{2\pi f X_C} \quad C = 0.000180 F.$$
$$C = 180.23 \mu F$$

$$\therefore R = 17.67 \Omega \quad \& \quad C = 180.23 \mu F.$$

2) $10 - j 15 \Omega$.

Soln : Compare ~~zeroes~~ ^{10-j15 with} $z = R - j X_L$

Wegel, $R = 10 \Omega$.

$$X_L = 15$$

$$X_C = \frac{1}{2\pi f C} \quad C = \frac{1}{2 \times 3.14 \times 50 \times 15}$$

$$C = \frac{1}{2\pi f C} \quad C = 0.00021231 F.$$
$$C = 212.31 \mu F$$

1. Purely Resistive AC Ckt :

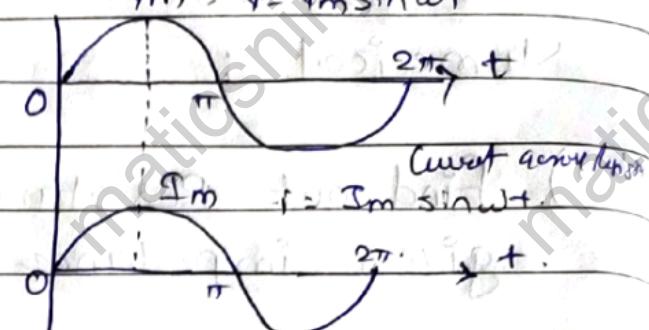
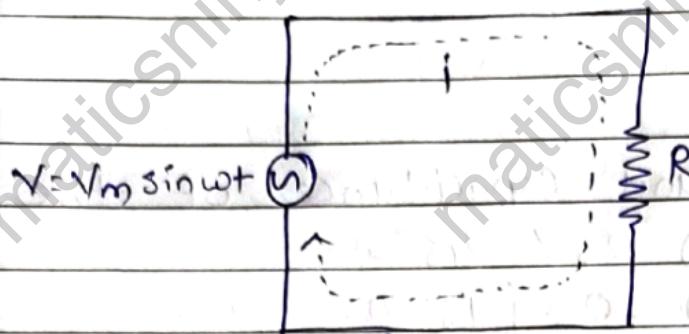


fig. @

fig. (b)

- The pure resistive ac ckt is as shown in above fig.
- It consist of an ac voltage source $V = V_m \sin \omega t$ & a Resistor R connected across it.
- The instantaneous current flowing through the ckt is i .

* Phasor Diagram :

v_{tg} & Current are in phase

- The phase diff. betn the v_{tg} & Current phasor is $\phi = 0$
- So, the v_{tg} & Current are in phase.

* v_{tg} & Current Equation :

- Referring to fig. (b) the instantaneous v_{tg} across resistor (V_R) is same as the source v_{tg} .
 $\therefore V_R = V = V_m \sin \omega t$.
- Applying the ohm's law the expression for instantaneous current flowing through resistor is given by ,

$$i = \frac{V_R}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m L_0}{R L_0}$$

$$\text{Let, } I_m = \frac{V_m}{R}, \quad f = \frac{V_m}{L_0} \cdot \frac{1}{2\pi} = \frac{V_m}{2\pi R L_0}$$

$$\therefore i = I_m \sin (\omega t)$$

* Impedance of the Purely Resistive Ckt:

- Impedance in Rec. form

$$Z = R + jX$$

↳ Reactive Part.
↳ Resistive Part.

- When the load is Purely Resistive then the reactive part is zero i.e. $X=0$, Hence. the impedance of Resistive ckt is given by.

$$Z = R \angle 0^\circ = (R + j0) \Omega$$

- In Polar form

$$Z = R \angle 0^\circ \Omega$$

* Power through Purely Res. Ckt

$$P = V_{rms} I_{rms}$$

Thus, the power in resistive ckt is equal to the product of rms value of v_{rg} & current.

Q.1) Write the expression for instantaneous current through pure ^{Resistance} resistive of value 100Ω if the source v_{rg} is $V(t) = 325 \sin(100\pi t + \frac{\pi}{3})$

Sol:- $v(t) = V_m \sin(\omega t + \phi)$
 $\therefore 325 \sin(100\pi t + \frac{\pi}{3})$

$$i = I_m \sin(\omega t + \phi)$$

$$I_m = \frac{V_m}{R} = \frac{325}{100} = 3.25 \text{ A}$$

$$\therefore i(t) = I_m \sin(\omega t + \phi)$$

$$\boxed{i(t) = 3.25 \sin(100\pi t + \frac{\pi}{3})}$$

$$Q.2) V(t) = 100 \sin(314t + \pi/2), R = 10 \Omega$$

$$V = V_m \sin(\omega t + \phi)$$


$$V = 100 \sin(314t + \pi/2)$$

$$i = I_m \sin(\omega t + \phi)$$

$$\therefore I_m = \frac{V_m}{R} = \frac{100}{10} = 10 \text{ A}$$

$$I(t) = 10 \sin(314t + \pi/2)$$

2. Purely Inductive AC Circuit:

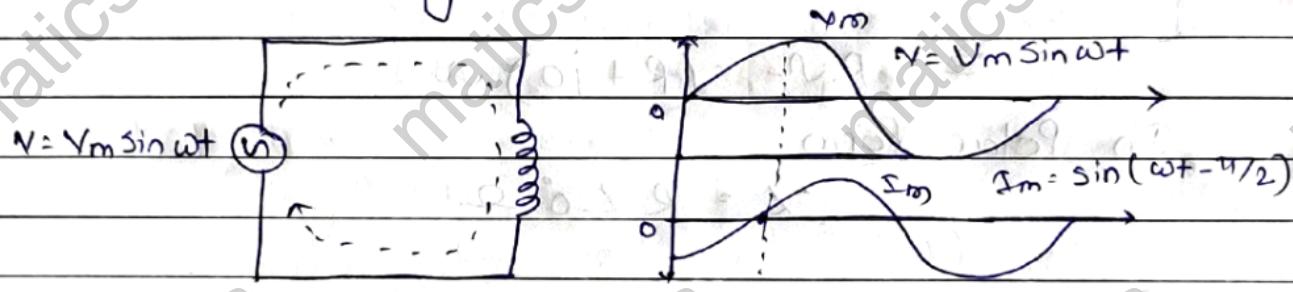


* 90° lag of current e.g.


$$V = V_m \sin \omega t, \quad \text{at } \phi = \frac{\pi}{2}, \quad \phi = \frac{\pi}{2}$$

$$i = I_m \sin(2\pi ft - \pi/2)$$
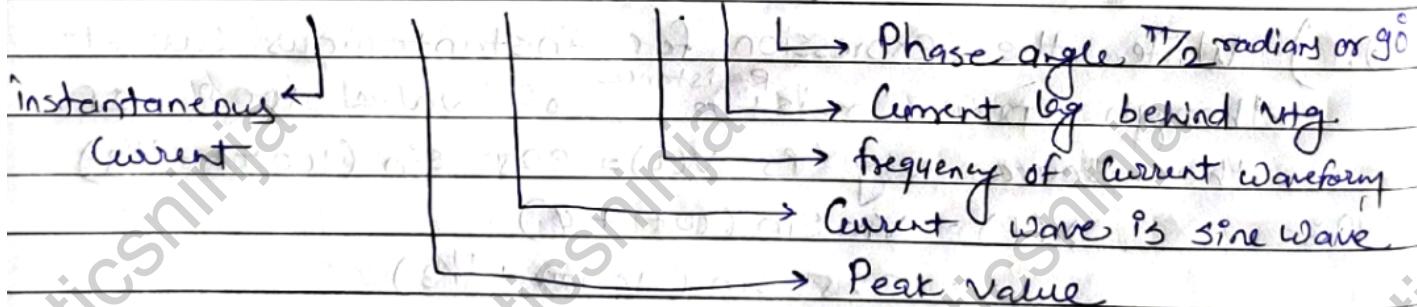
$$I_m = \frac{V_m}{X_L}, \quad X_L = 2\pi f L$$



* Phasor diagram:


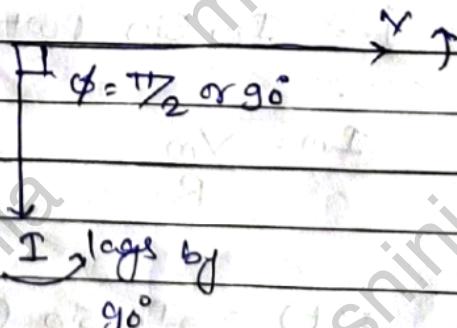


* Impedance of a Pure Inductive circuit:

- In rectangular form: $Z = R + jX_L$: $Z = jX_L$

- In Polar form: $Z = X_L \angle 90^\circ$

3. Purely Capacitive AC Circuit :

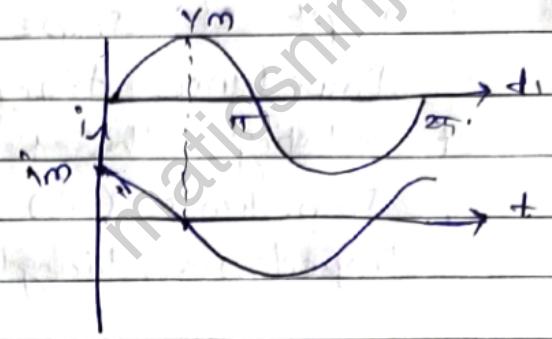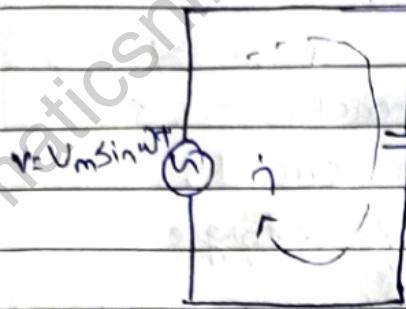

Vag F Current ωt .

$$V = V_m \sin \omega t.$$

$$I = I_m \sin (\frac{2\pi}{\omega} t + \frac{\pi}{2})$$

$$\frac{I_{\text{RMS}}}{V_{\text{RMS}}} = \frac{1}{X_C}$$

X_C

X_C

Current leads Vag

Phase diagram:

I leads by 90°

$\frac{\pi}{2}$ radians or 90°

V

$$\text{Impedance} = Z = R - j X_C$$

Rec. formy $R=0$.

$$\therefore Z = -j X_C$$

$$\text{In Polar form } Z = X_C \angle -90^\circ$$

Ex. ① Find the current through a purely capacitive circuit containing a V_{ag} source of $230V$, $50Hz$ & capacitor of $1000\mu F$.

Soln: RMS value of voltage $= 230V$, $f=50$, $C=1000\mu F$.
find : RMS value of current.

$$\text{RMS value of current} = \frac{V}{X_C}$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 1000 \times 10^{-6}} = 3.143 \Omega$$

$$I_{\text{RMS}} = \frac{230}{3.143} = 72.26 \text{ A.}$$

Chapter 2 Single Phase AC Series Circuit

* Concept of Impedance Triangle:

- Impedance triangle or is the graphical way of relating the resistance (R), reactance (X), & impedance (Z) of the given circuit.

Impedance triangle is right angle a triangle.

- The two side of impedance triangle


correspond to Resistance (R) & Inductance (X) with angle of 90° . betⁿ them third side.

The Correspond to magnitude of impedance

$$12) \text{ with } |Z|^2 = R^2 + X^2$$

$$R = |Z| \cos \phi, X = |Z| \sin \phi$$
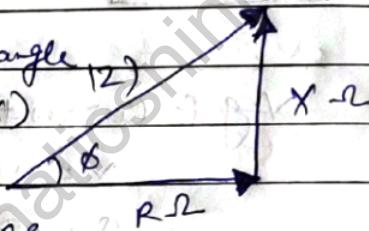
$$- \text{Phase Angle } \phi = \tan^{-1} (X/R)$$



* Important terms Related to Power

① Active, True, Real Power (P)

② Reactive, or imaginary Power (Q)

③ Apparent Power (S)

④ Power factor

1) Active Power : The truth power, real power & active power is defined as the Average power P_{av} consumed by the ac circuit is called as active power.

It is denoted by P

$$P = P_{av} = VI \cos \phi \text{ Watts.}$$

ϕ = Angle betⁿ V & Current

2) Reactive Power : Reactive Power is defined as the product of $V \phi$, I with sine of angle betⁿ V & I i.e ϕ .

It is denoted by Q

$$Q = VI \sin \phi \text{ VAR}$$

It is measured in VAR - Volt-Amp. Reactive

or kVAR

3) Apparent Power : Apparent power is defined as the product of the rms value of voltage & current. It is denoted by S .

measured in Volt-Amp. (VA) or kilovolt-Amp.
 $\therefore S = V \times I$

- It can be proved that apparent power is equal to the vector sum of active & reactive power.

$$S^2 = P^2 + Q^2 \quad S = \sqrt{P^2 + Q^2}$$

~~$P = V^2 R / Z$~~

~~$Q = V^2 X / Z$~~

4) Power Factor : It is the ratio of true power & the apparent power & it has no unit.

$$P.F. = \frac{\text{True Power}}{\text{Apparent Power}}$$

$$P.F. = \frac{VI \cos \phi}{VI}$$

$$\therefore P.F. = \cos \phi$$

from Impedance triangle $R = Z \cos \phi$

$$\cos \phi = \frac{R}{Z}$$

$$Z \cos \phi = Z \sin \phi =$$


$$\sin \phi = \frac{X_L}{Z}$$

$$\tan \phi = X_L / R$$

* Power Triangle :

= Power triangle is a graphically represents the all Active, Reactive & Apparent P/W.


$$\phi = \tan^{-1} (X/R)$$

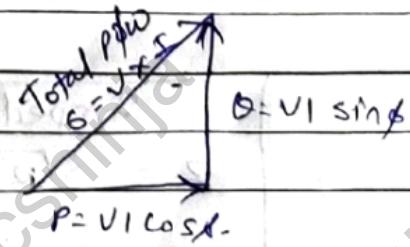


* AC Circuits with Series Elements :

- ① Series R-L Circuit
- ② Series R-C circuit
- ③ Series R-L-C circuit


1) Series R-L circuit :

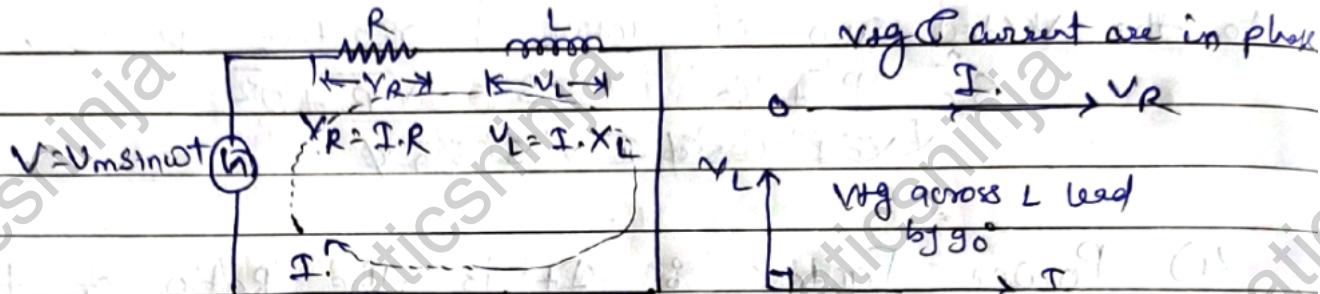

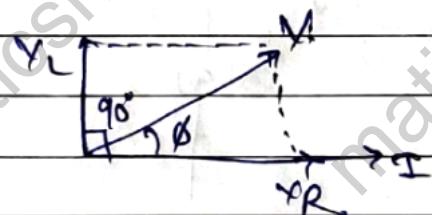
- In above fig. Shows the circuit diagram of R-L series cir.
 - When the resistance & inductance are connected in series with vtg or current source it is called as R-L Series cir.
- Voltage drop across R, $V_R = I \cdot R$ } in series $V = V_R + V_L$.
- $V_L = I \cdot X_L$



Phase Diagram of L-R-CR.

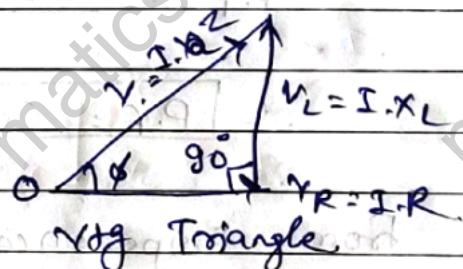

Impedance triangle.

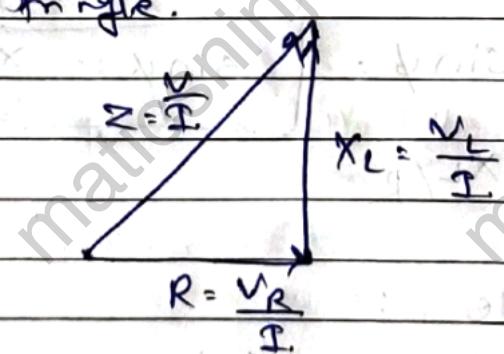

Divided both side by I .

Impedance in polar form

$$Z = \sqrt{R^2 + X_L^2}$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

Q.1) A circuit takes a current of 8A at 100V, the current lagging by 30° behind the applied voltage. Calculate, ① Impedance ② Resistance & ③ Inductance of the circuit with 50Hz frequency.

Soln:

Given, $I = 8A$, $V = 100V$, $\phi = 30^\circ$

Find, $Z = ?$, $R = ?$, $L = ?$

$$Z = \frac{V}{I} = \frac{100}{8} = 12.5 \Omega$$

$$\cos \phi = \frac{R}{Z} \quad (\therefore C \text{ from Impedance triangle})$$

$$R = Z \cos \phi$$

$$= 12.5 \cos(30^\circ)$$

$$R = 10.82 \Omega$$

$$X_L = 2\pi f L \quad \text{to find } X_L$$

$$\sin \phi = \frac{X_L}{Z} \quad (\therefore C \text{ from Impedance triangle})$$

$$X_L = Z \sin \phi$$

$$= 12.5 \sin(30^\circ)$$

$$X_L = 6.25 \Omega$$

$$X_L = 2\pi f L$$

$$L = \frac{X_L}{2\pi f} = \frac{6.25}{2 \times 3.14 \times 50} = 0.019 H$$

Q.2) An ohmic resistance is connected in series with a coil across 230V, 50Hz supply. The current is 1.8A and voltage across the resistance & coil are 80V & 170V respectively. calculate Resistance & Inductance of the coil.

Soln:

Given, $V = 230V$, $I = 1.8A$, $F = 50Hz$

$$V_R = 80V, V_L = 170V$$

Find, $R = ?$

$L = ?$

$$R = \frac{V_R}{I} = \frac{80}{1.8} = \underline{44.44 \Omega}$$




$$\text{Q.E.D. } L = \frac{X_L}{2\pi f}$$

$$X_L = \sqrt{Z^2 - R^2} \\ = \sqrt{(127.78)^2 - (44.44)^2} = 119.77 \Omega$$

$$|Z| = \frac{V}{I} = \frac{230}{1.8} = 127.78 \Omega$$

$$L = \frac{119.77}{2 \times 3.14 \times 50} = \underline{0.38 \text{ H}}$$

2) Series R-C Circuit

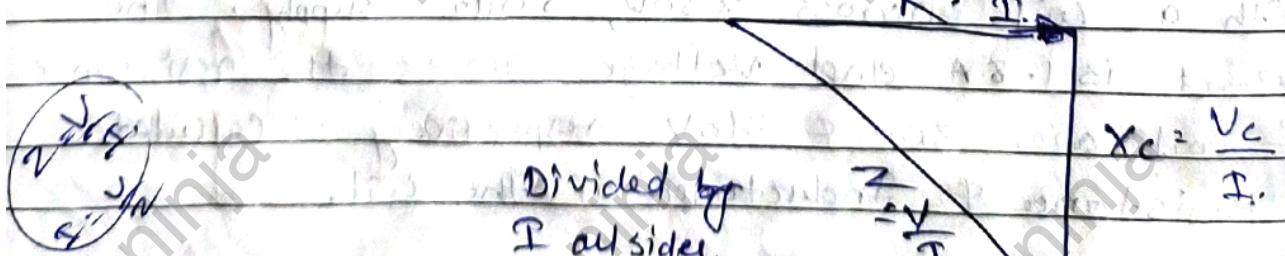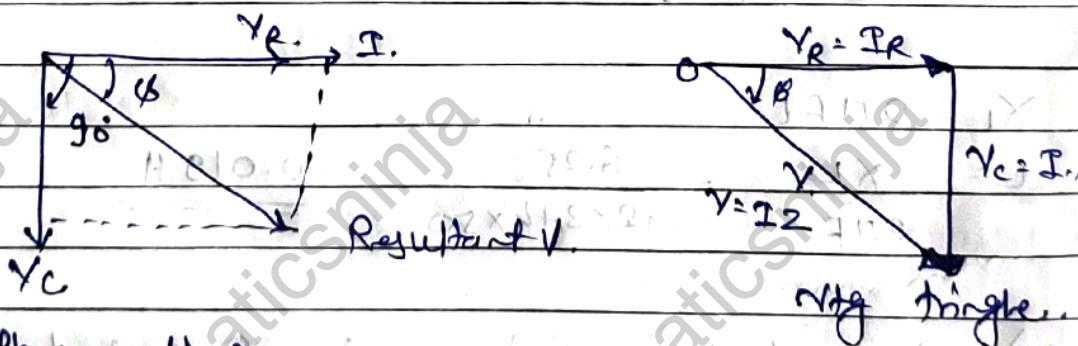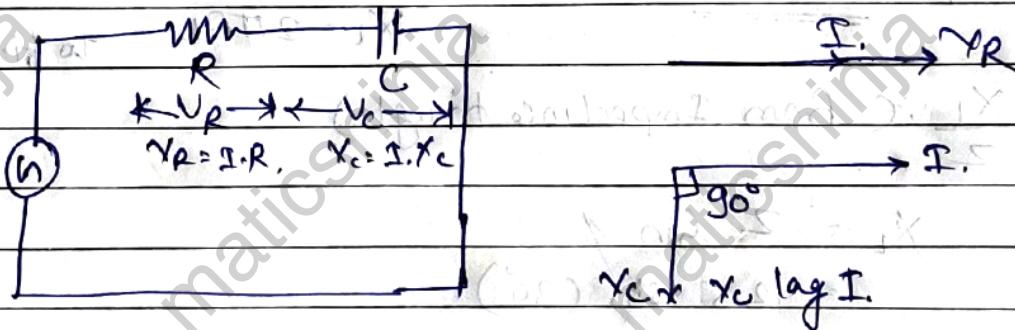

Impedance in Series R-C circuit.

$$Z = R - jX_C \quad \text{or} \quad Z = \sqrt{R^2 + X_C^2}$$

- In above fig. Shows the series connection with the combination of R & C.
- A pure capacitor (C) is connected in series with resistor, R & V_{tg} source of instantaneous voltage $V = V_m \sin \omega t$ is connected across the series combination of R & C.
- In case of series connection the applied voltage V is equal to the phasor addition of \bar{V}_R & \bar{V}_C .

\therefore Applied $V_{tg} = \bar{V} = \bar{V}_R + \bar{V}_C$ [Phasor Addition]

Numerical 06M

- ① A resistance of 100Ω & $50\mu F$ capacitor are connected in series across a $230V$, $50Hz$ Supply Find, ① Impedance ② The current flowing through circuit ③ Voltage Across Resistance & Capacitor ④ Power factor & Power.

Soln :

Given, $R = 100\Omega$, $C = 50\mu F$, $V = 230V$, $f = 50Hz$

$$= 50 \times 10^{-6} F$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 50 \times 10^{-6}} = 63.69 \Omega$$

$$Z = \sqrt{(100)^2 + (63.69)^2} \\ = 118.55 \Omega$$

$$Z = \frac{V}{I} \Rightarrow I = \frac{V}{Z} = \frac{230}{118.55} = 1.94 A.$$

$$V_R = I.R = 1.94 \times 100 = 194 \text{ V}$$

$$X_C = \frac{V}{I} \Rightarrow V_C = X_C \cdot I = 63.69 \times 1.94 = 123.55 \text{ V}$$

$$P.F = \cos \phi = \frac{R}{Z} = \frac{100}{118.55} = 0.84$$

$$\text{Power (P)} = VI \cos \phi$$

$$= 230 \times 1.94 \times 0.84$$

$$= 374.80 \text{ Watt}$$

$$\therefore Z = 118.55, V_R = 194V, V_C = 128.55, P.F = 0.8$$

$$I = 1.94, P = 374.80 \text{ Watt}$$

2) A resistance of 75Ω , $60\mu F$ are connected in series across $230V, 50Hz$ supply find:

- (1) X_C (2) Current (3) P.F (4) Active P/W.

Soln:

Given, $V = 230V, F = 50Hz, R = 75\Omega, C = 60\mu F$

Find: $X_C, I, P.F \& P$

$$X_C = \frac{1}{2\pi FC} = \frac{1}{2\pi \times 3.14 \times 50 \times 60 \times 10^{-6}} = 53.05\Omega$$

$$I = \frac{V}{Z} = \frac{230}{91.87} = 2.503 \text{ A.}$$

$$Z = \sqrt{(R)^2 + (X_C)^2}$$

$$= \sqrt{(75)^2 + (53.05)^2}$$

$$Z = 91.87 \Omega$$

$$\text{P.F Cos}\phi = \frac{R}{Z} = \frac{75}{91.87} = 0.816$$

$$P = VI \cos \phi$$

$$= 230 \times 2.503 \times 0.816$$

$$P = 469.76 \text{ Watt}$$

$$\therefore I = 2.503 \text{ A}, X_C = 53.05$$

$$\text{P.F: } 0.816, P: 469.76 \text{ W}$$

3) Find the expression for the current when V_{fg} represent by $V = 283 \sin(100\pi t)$ is applied to a coil having resistance is equal to 100Ω & capacitance $= 50\mu F$ also find power factor & frequency.

Soln: Given, $V_m = 283 \text{ V}$

$$i = I_m \sin \omega t + \phi$$

$$\omega = 100\pi$$

$$R = 100\Omega \text{ & } C = 50 \times 10^{-6} \text{ F.}$$

$$\text{P.F.} = \cos \phi = \frac{R}{Z} = \frac{100}{118.55} = 0.84 \quad \phi = \cos^{-1}(0.84) = 32.85^\circ$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{(100)^2 + (63.69)^2} = 118.55$$

$$X_C = \frac{1}{2 \times 3.14 \times 50 \times 50 \times 10^{-6}} = 63.69 \Omega$$

$$\omega = 2\pi f$$

$$100\pi = 2\pi f$$


$$f = \frac{100\pi}{2\pi} = 50 \text{ Hz}$$

$$I_m = \frac{V_m}{Z} = \frac{283}{118.55} = 2.38$$

$$i = I_m \sin(\omega t + \phi)$$

$$i = 2.38 \sin(100\pi t + 32.85^\circ)$$

Series R-L-C circuit :

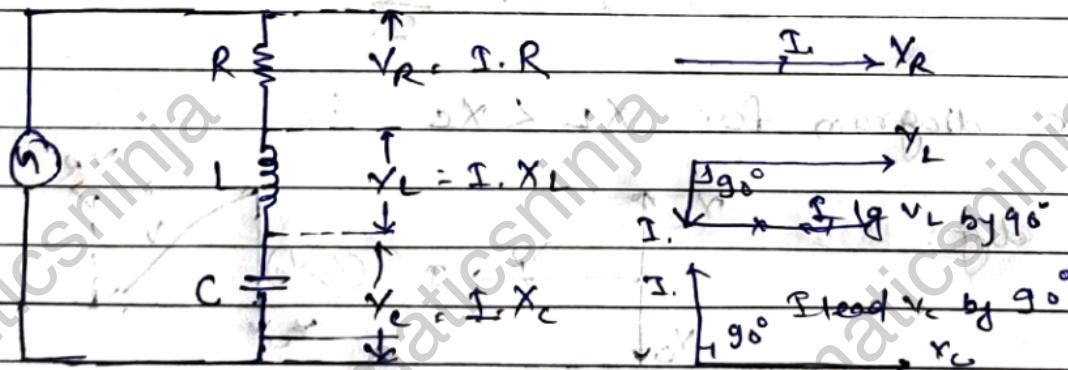

$$\vec{V} = \vec{V}_R + \vec{V}_L + \vec{V}_C$$

$$\vec{V} = I \vec{R} + (I \vec{X}_L) + (I \vec{X}_C)$$

$$\vec{V} = I (R + X_L + X_C)$$

$$I = \frac{\vec{V}}{R + j(X_L + X_C)}$$

$$I = \frac{V}{Z} \quad (\text{we got value of } I)$$


Where, V_R , V_L & V_C are V_{fg} across Resistance, Induct & Capacitor respectively.

Phasor diagram :


- ① Condition 1st : $X_L > X_C$
- ② Condition 2nd : $X_L < X_C$
- ③ Condition 3rd : $X_L = X_C$

① Phasor diagram for $X_L > X_C$:


Phasor dig :

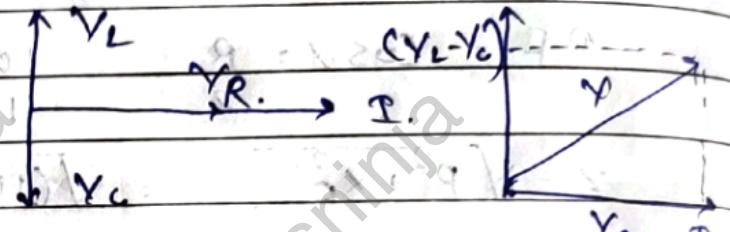


Voltage triangle :

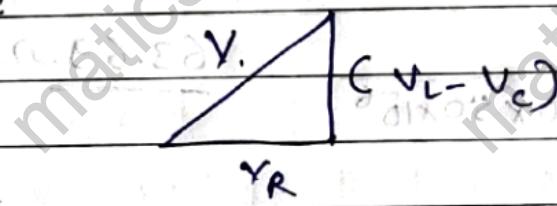

Power triangle :

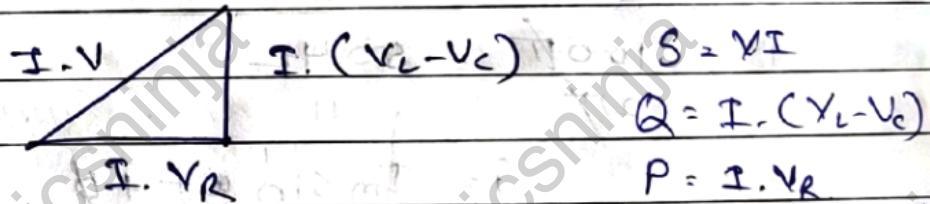


Impedance triangle :

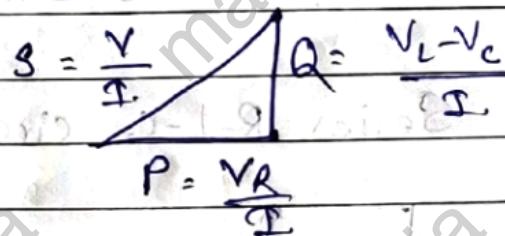


② Phasor diagram for $X_L < X_C$:


Phasor dig :

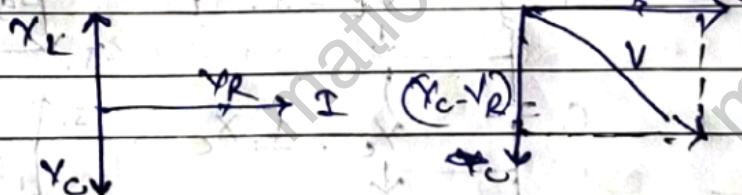


Voltage triangle :

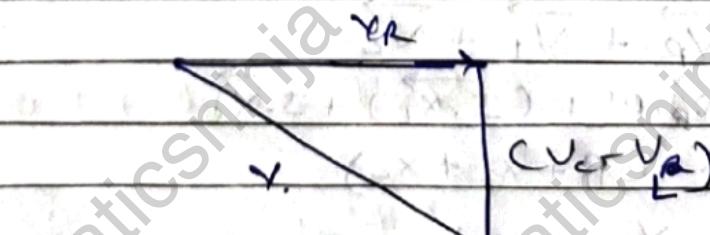

P/W triangle:

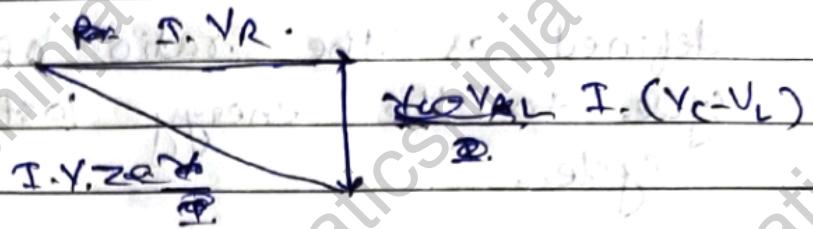


Impedance Triangle:

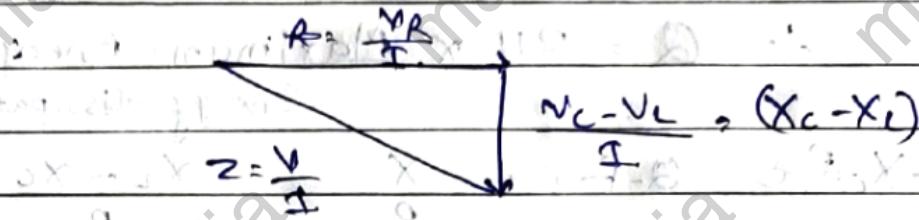

$$Z = R + jX$$

$$Z = \sqrt{R^2 + (X_c - X_L)^2}$$

③ Phasor dig. for $X_L = X_c$

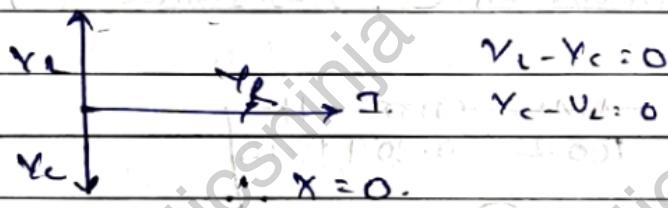

$$\therefore Z = R + jX$$

$$Z = \sqrt{R^2 + 0^2} = R$$

$$\therefore |Z| = R$$

Power factor :

Sl. No.	Case	Nature of RLC Circ.	Power factor
1	$X_L > X_c$	R-L series	Lagging & less than 1
2	$X_c > X_L$	R-C series	Leading & less than 1
3	$X_L = X_c$	Purely Resistive	1

* Q. Factor : The Q (Quality) factor is defined as the ratio of energy stored per cycle to the energy lost (or dissipated) per cycle.


$\therefore Q = \frac{2\pi \times \text{Maximum Energy stored per cycle}}{\text{Energy dissipated per cycle}}$

$$X_L > X_C \quad Q.F. = \frac{X_L}{R} = \frac{X_L - X_C}{R}$$

$$X_C > X_L \quad Q.F. = \frac{X_C}{R} = \frac{X_C - X_L}{R}$$

* Numericals :

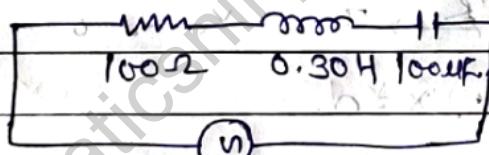1) From Given crt find Impedance, Current, V_{tg} across Inductance, Resistance &, Capacitance & P.F.



$$V = 200 \sin(100\pi t)$$

Soln :- Given, R = 100Ω, L = 0.30H, C = 100μF, V_m = 200V, Find : Z, I, V_L, V_R, V_C & P.F. $\omega = 100\pi$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 0.30 = 94.2 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 100 \times 10^{-6}} = 31.8 \Omega$$

$$Z = \sqrt{100^2 + (94.2 - 31.8)^2} = 117.8 \Omega$$

$$I = \frac{V}{Z} = \frac{200}{117.8} = 1.69 \text{ A.}$$

$$V_L = I \cdot X_L$$

$$= 1.69 \times 94.2$$

$$= 159.19 \text{ V}$$

$$V_R = I \cdot R = 1.69 \times 100 = 169 \text{ V}$$

$$V_C = I \cdot X_C = 1.69 \times 31.8 = 53.74 \text{ V}$$

$$\text{P.F} = \cos \phi = \frac{R}{Z} = \frac{100}{117.87} = 0.84$$

2) A series circuit having pure resistance of 40Ω & Inductance of 50.07 mH & capacitor is connected across 400V , 50Hz , AC supply. This R-L-C combination draws a current of 10A . calculate:

- (1) P.F of the circuit (2) Capacitor value.

Soln :-

Given, $R = 40\Omega$, $L = 50.07 \text{ mH}$, $V = 400\text{V}$, $f = 50$, $50.07 \times 10^{-3} \text{ H}$, $I = 10\text{A}$.

Find : P.F & C.

$$\text{P.F} = \cos \phi = \frac{R}{Z} = \frac{40}{40} = 1$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{40^2 + (15.72 - 15.72)^2} = 40\Omega$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 50.07 \times 10^{-3} = 15.72 \Omega$$

According to 3rd condition $X_L = X_C$

$$\therefore X_C = 15.72 \Omega$$

$$X_C = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2 \times 3.14 \times 50 \times 15.72} = 0.000202 \text{ or } 2.02 \times 10^{-4} \text{ or } 202 \times 10^{-6} \text{ F}$$

$$T = \frac{V}{Z} = \frac{400}{40} = 10 \text{ s}$$


$$202 \mu\text{F}$$

3) A coil has resistance of 10 ohm & Inductance of 0.12733 H. This coil is connected in series with a capacitor of 230 μF across the source of supply of 230V, 50 Hz. Find :

- ① X_L
- ② X_C
- ③ γ_{tg} across coil & capacitor
- ④ P.F.
- ⑤ Z
- ⑥ Current
- ⑦ Angle of phase displacement betw γ_{tg} & current.

Soln:

10 Ω 0.12733 230 μF

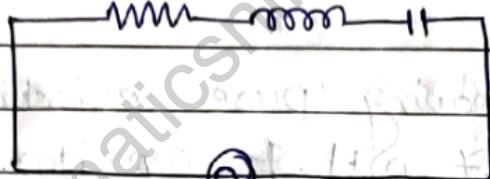

Given from circ diag.
R, L, C & V, F.

$$\textcircled{1} \quad X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 0.12733 = 40 \Omega$$

$$\textcircled{2} \quad X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 230 \times 10^{-6}} = 13.83 \Omega$$

$$\textcircled{3} \quad V_L = I \cdot X_L = 8.21 \times 40 = 328 V$$

$$\textcircled{4} \quad I = \frac{V}{Z} = \frac{230}{28} = 8.21 A.$$

$$\textcircled{5} \quad Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{10^2 + (40 - 13.83)^2} = 28 \Omega$$

$$\textcircled{6} \quad V_C = I \cdot X_C = 113.54 V$$

$$\textcircled{7} \quad \text{P.F.} = \cos \phi = \frac{R}{Z} = \frac{10}{28} = 0.35$$

$$\textcircled{8} \quad \phi = \tan^{-1} \left(\frac{X}{R} \right) = \tan^{-1} \left(\frac{26.17}{10} \right) = 69.08^\circ$$

$$X = X_L - X_C$$

$$X = 26.17$$

* Resonance Frequency : The frequency at which inductive Reactance becomes equal to the Capacitive Reactance is called as resonance frequency.

$$XL = XC$$

$$2\pi f L = \frac{1}{2\pi f C}$$

$$f_r \times f_r^2 = \frac{1}{2\pi \times 2\pi L \cdot C}$$

$$f_r^2 = \frac{1}{4\pi^2 L \cdot C}$$

$$f_r = \sqrt{\frac{1}{4\pi^2 L \cdot C}}$$

$$f_r = \frac{1}{2\pi \sqrt{L \cdot C}}$$

(formula for Resonance frequency)

At Resonant $P_f = R$

Q - Factor of R-L-C series circuit :

The Q-factor of series resonant circuit is also defined as the voltage magnification provided by the circuit at its resonant frequency.

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{V_L}{V}$$

$$\frac{X_L \times X_C}{X \cdot R}$$

$$\frac{X_L}{R}$$

$$= \frac{2\pi f r L}{R}$$

$$= \frac{2\pi}{2\pi f r C} \frac{L}{R}$$

, Taking square root

$$Q = \sqrt{\frac{1}{R^2} \frac{L}{C}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

∴ formula for Q

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\text{Taking square root}$$


$$\left(\frac{1}{R^2}\right) \frac{L}{C}$$

$$= \frac{1}{X_C} \times \frac{L^2}{R^2}$$

Numerical on Resonant Frequency :

1) A circuit consisting of a coil of Resistance 12Ω & Inductance 0.15 H in Series with Capacitance of $12\text{ }\mu\text{F}$ is connected to a Variable Frequency Supply which has a constant $V_{\text{eff}} 240\text{ V}$. Calculate : ① Resonant frequency ② Current in A .

Solⁿ :

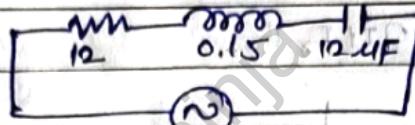

Given,

$$R = 12\Omega, L = 0.15\text{ H}, C = 12\text{ }\mu\text{F}$$

Find : f_r & I .

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.15 \times 12 \times 10^{-6}}} = 118.63\text{ Hz}$$

At Resonant $\omega_1 = R$ $\therefore \omega = 12$

$$I = \frac{V}{R} = \frac{240}{12} = 20\text{ A.}$$

2) An AC series circuit having $R = 10\Omega$, $L = 0.1\text{ H}$, $C = 100\text{ }\mu\text{F}$ is connected to $230\text{ V}, 50\text{ Hz}$ supply find
① Resonance frequency ② Quality factor ③ I

Solⁿ:

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 100 \times 10^{-6}}} = 50.35\text{ Hz}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{0.1}{100 \times 10^{-6}}} = 3.16$$

$$I = \frac{V}{R/2} = \frac{230}{10} = 23\text{ A.}$$