

Unit-2 : Single Phase AC Parallel Circuit

A.C. Parallel Circuit :

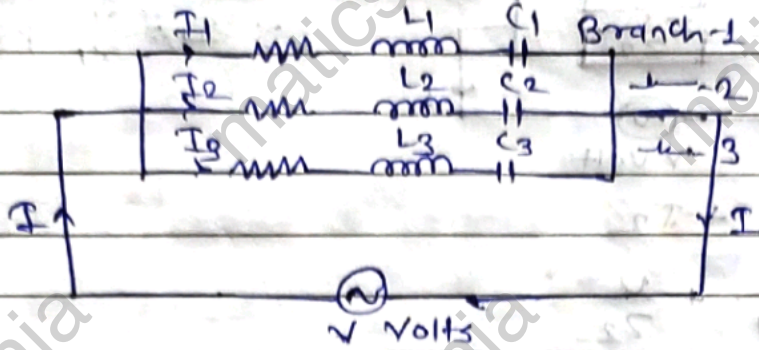


fig. Parallel AC circuit

Defn : A parallel ac circuit has two or more series circuits connected in parallel with each other across a common alternating voltage source. is called as parallel AC ckt.

- Each series ckt is called as a branch in the parallel ckt.
- Let, The current flowing through the three branches be I_1 , I_2 & I_3 respectively. As the vtg drop across all the branches is the same i.e V Volts. These current are given by the following expression.

$$I_1 = \frac{V}{Z_1}, I_2 = \frac{V}{Z_2} \text{ \& } I_3 = \frac{V}{Z_3}$$

Applying KCL & using phasor Addition of we get,

$$\overline{I} = \overline{I_1} + \overline{I_2} + \overline{I_3}$$

Substitute Value of I we get,

$$\frac{V}{Z} = \frac{V}{Z_1} + \frac{V}{Z_2} + \frac{V}{Z_3}$$


$$\frac{V}{Z} = V \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right)$$

$$\frac{V}{Z \cdot V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\boxed{\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

Above eqⁿ shows the equivalent expression Impedance of the parallel ckt.

Two Impedance in Parallel :

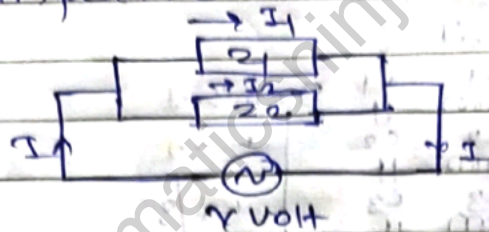

$$I = I_1 + I_2$$

$$I = I_1 + I_2$$

$$\frac{V}{Z} = \frac{V}{Z_1} + \frac{V}{Z_2}$$

$$\frac{V}{Z} = V \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right)$$

$$\frac{V}{Z} = \frac{V}{Z_1} + \frac{V}{Z_2}$$

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\frac{1}{Z} = \frac{Z_1 + Z_2}{Z_1 \cdot Z_2}$$

$$\boxed{Z = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2}}$$

Addition & Subtraction of Impedance :

$$Z_1 = R_1 + jX_1$$

$$Z_2 = R_2 + jX_2$$

$$Z_1 + Z_2 = (R_1 + jX_1) + (R_2 + jX_2)$$

$$= (R_1 + R_2) + j(X_1 + X_2)$$

Similarly

$$Z_1 - Z_2 = (R_1 + jX_1) - (R_2 + jX_2)$$

$$= (R_1 - R_2) - j(X_1 - X_2)$$

Multiplication & Division of Impedance :

$$Z_1 \cdot Z_2 = (R_1 + jX_1)(R_2 + jX_2) \angle \phi_1 + \phi_2$$

$$\frac{Z_1}{Z_2} = \frac{Z_1}{Z_2} \angle \phi_1 - \phi_2$$

Numerical on Addition, subtraction, Multiplication & Division

1) Find the value of $Z = \frac{(3+j4) \cdot 5 \angle 30^\circ}{(6+j8)}$

in rectangular form.

Solⁿ:

$$Z = \frac{(3+j4) \cdot 5 \angle 30^\circ}{(6+j8)}$$

Convert $(3+j4)$ & $(6+j8)$ in polar form

$$\therefore Z = \frac{(5 \angle 53.13^\circ) \times (5 \angle 30^\circ)}{(10 \angle 53.13^\circ)}$$

$$Z = \frac{25 \angle 83.13^\circ}{10 \angle 53.13^\circ}$$

$$Z = 2.5 \angle 30^\circ \quad \therefore Z = [2.16 + j1.25]$$

2) If $A = 4+j7$, $B = 8+j9$ & $C = 5-j6$ then calculate:

- ① $\frac{A+B}{C}$ ② $\frac{A \cdot B}{C}$ ③ $\frac{A+B}{B+C}$ ④ $\frac{B-C}{A}$

Solⁿ:

$$\text{① } \frac{A+B}{C} = \frac{(4+j7) + (8+j9)}{(5-j6)} = \frac{12+j16}{5-j6} = \frac{20 \angle 53.13^\circ}{7.81 \angle -50.19^\circ} = 2.56 \angle 103.32^\circ$$

$$\text{② } \frac{A \cdot B}{C} = \frac{(8 \angle 60^\circ) \cdot (12 \angle 48.36^\circ)}{7.81 \angle -50.19^\circ} \quad \text{Converted into Polar}$$

$$= \frac{96 \angle 108.36^\circ}{7.81 \angle -50.19^\circ} = 12.29 \angle 158.55^\circ$$

$$\text{③ } \frac{A+B}{B+C} = \frac{(4+j7) + (8+j9)}{(8+j9) + (5-j6)} = \frac{12+j16}{13+j3} = \frac{20 \angle 53.13^\circ}{13.34 \angle 12.99^\circ} = 1.49 \angle 40.14^\circ$$

$$\textcircled{4} \quad \frac{B-C}{A} = \frac{(8+j9) - (5-j6)}{(4+j7)} = \frac{3+j15}{4+j7} = \frac{15.29 \angle 78.69^\circ}{8.06 \angle 60.25^\circ} = 1.89 \angle 18.44^\circ$$

3) Find $Z = \frac{(5+j8)}{(7+j9)}$ in Rectangular form

$$\text{Soln: } Z = \frac{(5+j8)}{(7+j9)} = \frac{9.43 \angle 57.99^\circ}{11.40 \angle 52.12^\circ} = 0.82 \angle 5.87^\circ$$

$$\boxed{Z = 0.81 + j0.08}$$

4) If $Z_1 = 3+j7$ & $Z_2 = 12-j16$ are connected in parallel find the equivalent Impedance of Combination.

$$\text{Soln: Given } Z_1 = 3+j7, Z_2 = 12-j16$$


$$Z_1 = 3+j7 = 7.61 \angle 66.80^\circ$$

$$Z_2 = 12-j16 = 20 \angle -53.13^\circ$$

$$Z_{eq} = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} = \frac{(7.61 \angle 66.80^\circ)(20 \angle -53.13^\circ)}{(3+j7) + (12-j16)} = \frac{152.2 \angle 13.67^\circ}{15-j9} = \frac{152.2 \angle 13.67^\circ}{17.49 \angle -30.96^\circ} = 8.70 \angle 44.63^\circ$$

$$\boxed{Z_{eq} = 6.19 + j6.11}$$

R-L Parallel Circuit :

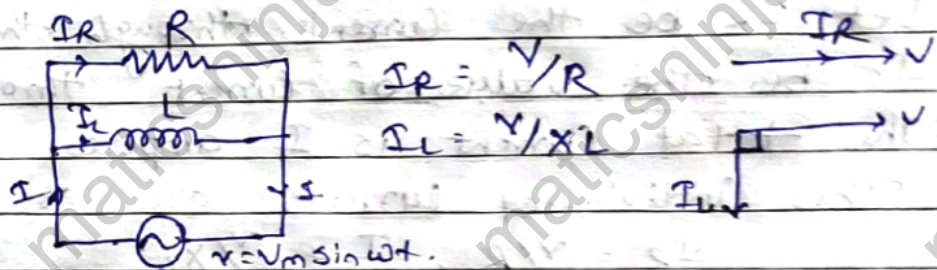


- In above fig. Shows the parallel R-L circuit.
- The AC voltage source of instantaneous $v(t) = V_m \sin \omega t$ has been connected across the parallel combination of L & R.
- Let I_R be the current through the resistance & I_L be the current through the inductor. The total current is I amperes.

- The individual currents are as follows :

$$I_R = V/R, \quad I_L = V/X_L$$

Where, V = RMS value of supply $v(t)$.

* Phasor diagram :

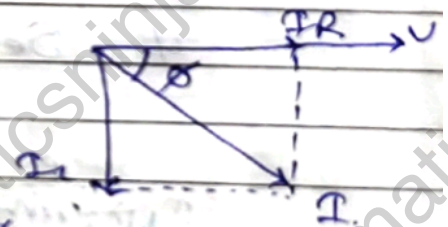


- The supply current I is equal to the phasor addition of I_R & I_L .

$$\therefore \vec{I} = \vec{I_R} + \vec{I_L}$$

$$\therefore \frac{V}{R} + \frac{V}{X_L}$$

R-C Parallel Circuit :

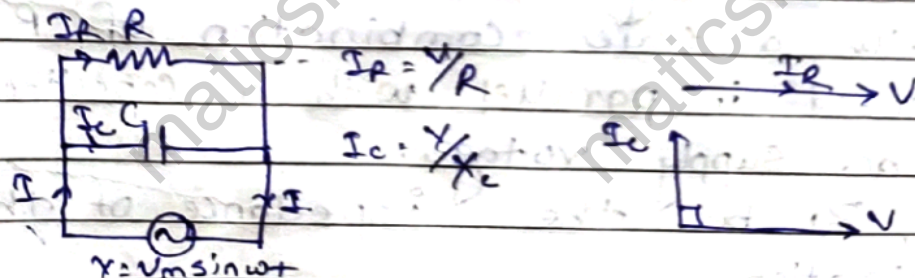

- In above fig. Shows the parallel R-C circuit with an AC excitation.
- A pure capacitor of value C is connected in parallel with a resistor R & a voltage source of instantaneous $v(t) = V_m \sin \omega t$ is connected across the parallel combination of R & C.

- Let I_R be the current through the resistance & I_C be the value of current through capacitor. The total current is I - ampere.


- The individual currents are as follows:

$$I_R = V/R, \quad I_C = V/X_C$$

where, V = rms value of supply voltage

* Phasor diagram :

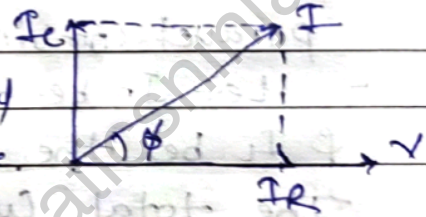
- The supply current I is equal to the phasor addition of I_R & I_C .



$$\vec{I} = \vec{I_R} + \vec{I_C}$$


$$= \frac{V}{R} + \frac{V}{X_C}$$

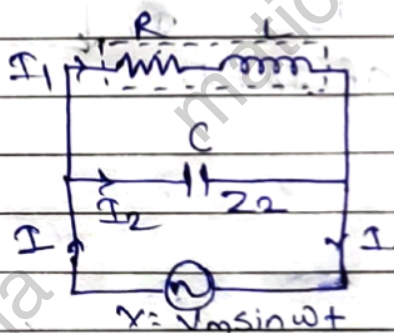* Series Combination of R & L in Parallel with Capacitor :



$$I_1 = \frac{V}{Z_1}$$

$$I_2 = \frac{V}{X_C}$$

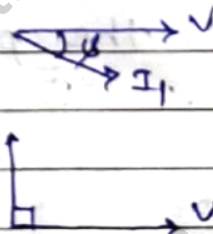

- In above fig. shows the AC parallel circuit in which a series combination of R & L is connected in parallel with a capacitor C across the ac supply voltage.

- Let, Z_1 be the impedance of the RL series combination.

$$Z_1 = R + jX_L = |Z_1| \angle \phi_1$$

- Let Z_2 be the impedance of the branch containing the capacitor.

$$Z_2 = 0 - jX_C = |Z_2| \angle \phi_2$$


- The individual currents are given by

$$I_1 = \frac{V}{Z_1}, \quad I_2 = \frac{V}{Z_2}$$

where, V = RMS value of supply voltage

* Phasor diagram :

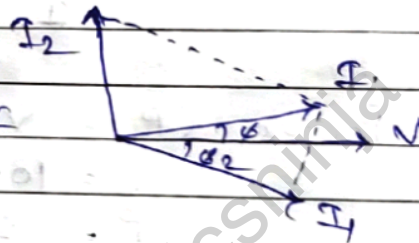- The supply current I is equal to the phasor addition of I_1 & I_2 .



$$\therefore \underline{I} = \underline{I_1} + \underline{I_2}$$

$$= \frac{V}{Z_1} + \frac{V}{Z_2}$$


Example 1
Numerical :

1) A coil having resistance of 5Ω & Inductance of 0.2 H is arranged in parallel with another coil having resistance of 1Ω & Inductance of 0.08 H . Calculate the current through the combination & Power absorbed when a voltage of 100 V , 50 Hz is applied. Use impedance method.

Soln :

Coil 1 : $R_1 = 5\Omega$, $L_1 = 0.2\text{ H}$

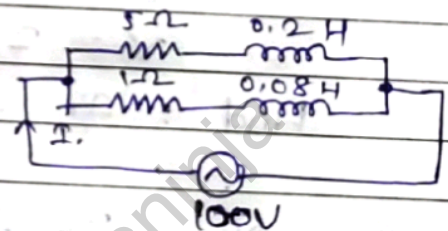Coil 2 : $R_2 = 1\Omega$, $L_2 = 0.08\text{ H}$



For coil 1 :

$$X_1 = 2\pi f L_1 = 2 \times 3.14 \times 50 \times 0.2 = 62.84\Omega$$

$$Z_1 = R_1 + jX_1 = 5 + j62.84 = 63.03 \angle 85.45^\circ$$

For coil 2 :

$$X_2 = 2\pi f L_2 = 2 \times 3.14 \times 50 \times 0.08 = 25.12\Omega$$

$$Z_2 = R_2 + jX_2 = 1 + j25.12 = 25.13 \angle 87.72^\circ$$

$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(63.03 \angle 85.45^\circ) \times (25.13 \angle 87.72^\circ)}{(63.03 \angle 85.45^\circ) + (25.13 \angle 87.72^\circ)}$$

$$= \frac{1583.94 \angle 173.17^\circ}{(5 + j62.84) + (1 + j25.12)}$$

$$= \frac{1583.94 \angle 173.17^\circ}{88.6 + j87.96} = \frac{1583.94 \angle 173.17^\circ}{88.16 \angle 86.09^\circ}$$

$$Z_{eq} = 17.96 \angle 87.09^\circ$$

$$\text{Total Current (I)} = \frac{V}{Z_{eq}} = \frac{100 \angle 0^\circ}{17.96 \angle 87.09^\circ}$$

$$I = 5.56 \angle -87.09^\circ \text{ Amp.}$$

$$\begin{aligned} \text{Power (P)} &= VI \cos \phi \\ &= 100 \times 5.56 \times \cos(-87.08^\circ) \\ P &= 28.3 \text{ W} \end{aligned}$$

$$I = 5.56 \angle -87.09^\circ \text{ Amp} \quad \& \quad P = 28.3 \text{ W}$$

Same as ⑤

2) Two Impedance $Z_1 = 8 + j6 \, \Omega$ & $Z_2 = 4 + j4$ are connected in parallel across 200V, 50 Hz AC supply. Calculate: ① Branch Current (I_1) ② Branch Current (I_2) ③ Total Current (I_T) Draw the phasor diagram.

Soln:


$$Z_1 = 8 + j6 = 10 \angle 36.85^\circ$$

$$Z_2 = 4 + j4 = 5.65 \angle 45^\circ$$

$$V = 200 \text{ V}, \quad f = 50 \text{ Hz}$$

Find: I_1 , I_2 & I_T with Phasor diagram.
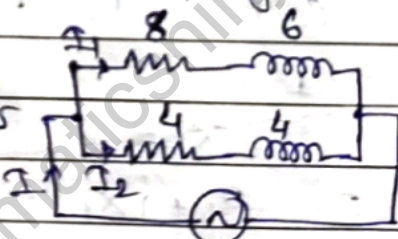
$$I_T = \frac{V}{Z_{eq}} = \frac{200 \angle 0^\circ}{3.61 \angle 42.05^\circ} = 55.29 \angle -42.05^\circ$$



$$Z_{eq} = Z_1 \parallel Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(10 \angle 36.85^\circ) \times (5.65 \angle 45^\circ)}{(8 + j6) + (4 + j4)}$$

$$= \frac{56.5 \angle 81.86^\circ}{12 + j10}$$


$$= \frac{56.5 \angle 81.86^\circ}{15.62 \angle 39.8^\circ}$$

$$Z_{eq} = 3.61 \angle 42.05^\circ$$


$$\text{Branch Current } (I_1) = \frac{V}{Z_1} = \frac{200 \angle 0^\circ}{10 \angle 36.85^\circ} = 20 \angle -36.85^\circ \text{ A}$$

$$\text{Branch Current } (I_2) = \frac{V}{Z_2} = \frac{200 \angle 0^\circ}{5.65 \angle 45^\circ} = 35.39 \angle -45^\circ \text{ A}$$

Phasor diagram :

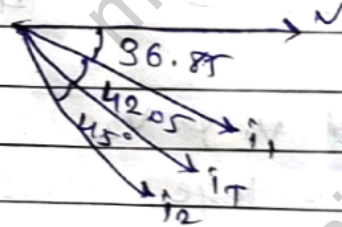

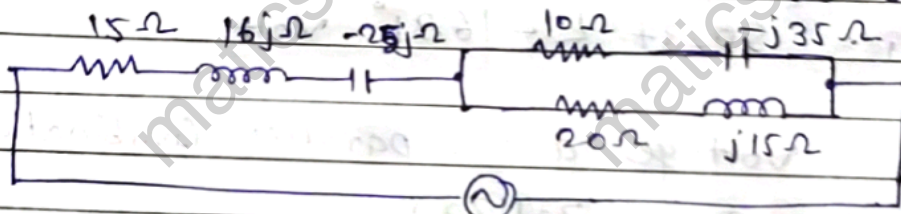3) Find I , V_1 , ϕ , V_2 for the circuit as shown in fig.



120V, 50Hz

Soln: $V = 120V$,

$$\text{Let } Z_1 = 15 + j(16 - 25)$$

$$= (15 - j9) = 17.49 \angle -30.96^\circ \Omega$$

$$Z_2 = 10 - j35 = 36.4 \angle -74^\circ \Omega$$

$$Z_3 = 20 + j15 = 25 \angle 36.86^\circ \Omega$$

Find Total impedance Z :

$$Z = Z_1 + (Z_2 || Z_3) \quad \text{--- (1)}$$

$$Z_2 || Z_3 = \frac{Z_2 \cdot Z_3}{Z_2 + Z_3} = \frac{(36.4 \angle -74^\circ)(25 \angle 36.86^\circ)}{10 - j35 + 20 + j15}$$

$$= \frac{910 \angle -37.14^\circ}{30 - j20}$$

$$= \frac{910 \angle -37.14^\circ}{36 \angle -33.69^\circ}$$

$$\therefore Z_2 || Z_3 = 25.27 \angle -3.45^\circ$$

$$Z_2 || Z_3 = 25.22 - j1.52 \quad \text{--- (2)}$$

Substituting Eqⁿ (2) in Eqⁿ (1) we get,

$$Z = Z_1 + (Z_2 || Z_3)$$

$$= 15 - j9 + 25.22 - j1.52$$

$$\therefore Z = 40.22 - j10.52 = 41.57 \angle -14.65^\circ$$

Find total current (I) :

$$I = \frac{V}{Z} = \frac{120 \angle 0^\circ}{41.57 \angle -14.65^\circ} = 2.88 \angle 14.65^\circ \text{ A.}$$

Find V_1 & V_2 :

V_1 : Voltage across Z_1

$$= I \times Z_1$$

$$= (2.88 \angle 14.65^\circ) \times (17.49 \angle -30.96^\circ)$$

$$V_1 = 50.37 \angle -16.31^\circ \text{ Volt}$$

V_2 : Voltage across parallel combination of Z_2 & Z_3

$$= I \times (Z_2 || Z_3)$$

$$= (2.88 \angle 14.65^\circ) \times (25.27 \angle -3.45^\circ)$$

$$V_2 = 72.77 \angle 11.2^\circ \text{ Volt.}$$

4) A choke coil has a resistance of 2Ω & an inductance of 0.035 H is connected in parallel with a $350 \mu\text{F}$ capacitor which is in series with a resistance of 20Ω . When the combination is connected across a 200V , 50 Hz supply, Calculate :


- ① Total current taken
- ② Power factor of whole ckt.

Soln : Given,

$$R_1 = 2 \Omega \quad L = 0.035$$

$$R_2 = 20 \Omega \quad C = 350 \times 10^{-6} \text{ F}$$

$$I = \frac{V}{Z_{eq}}$$

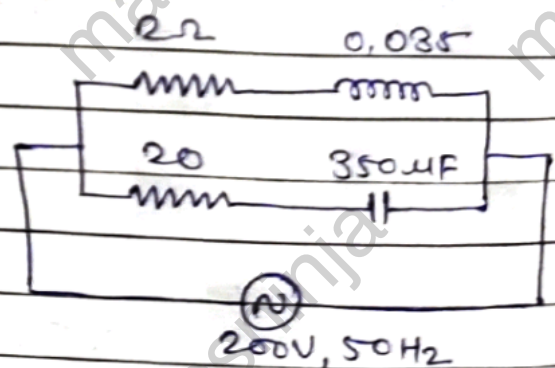

$$Z_{eq} = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2}$$

$$Z_1 = R_1 + jX_L$$

$$X_L = 2\pi fL = 2 \times 3.14 \times 50 \times 0.035 = 11 \Omega$$

$$Z_1 = 2 + j11 = 11.18 \angle 79.69^\circ$$

$$Z_2 = R_2 + jX_C$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.14 \times 50 \times 350 \times 10^{-6}} = 9.09 \Omega$$

$$Z_2 = 20 - j9.09 = 21.96 \angle -24.44^\circ$$

$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(11.18 \angle 79.69^\circ)(21.96 \angle -24.44^\circ)}{2 + j11 + 20 - j9.09}$$

$$= \frac{245.51 \angle 55.25^\circ}{22 + j1.91}$$

$$= \frac{245.51 \angle 55.25^\circ}{22.08 \angle 4.96^\circ}$$

$$Z_{eq} = 11.11 \angle 50.29^\circ$$


$$I = \frac{200 \angle 0^\circ}{11.11 \angle 50.29^\circ} = 18 \angle -50.29^\circ \text{ A}$$

$$\text{Power Factor} = \cos \phi$$

$$= \cos (-50.29^\circ)$$

$$= 0.63 \text{ lagging}$$

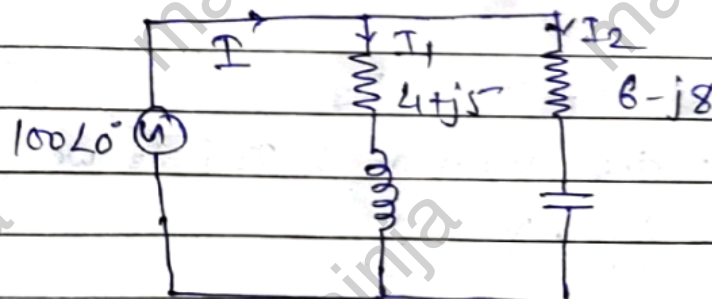5) Calculate current I_1 , I_2 & total current I in the ckt shown.



Soln

$$Z_1 = 4 + j5 = 6.4 \angle 51.34^\circ$$

$$Z_2 = 6 - j8 = 10 \angle -53.13^\circ$$

$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(6.4 \angle 51.34^\circ)(10 \angle -53.13^\circ)}{4 + j5 + 6 - j8}$$

$$= \frac{64 \angle -1.79^\circ}{10 - j3} = \frac{64 \angle -1.79^\circ}{10.44 \angle -16.69^\circ}$$

$$\therefore Z_{eq} = 6.13 \angle 14.9^\circ \Omega$$

$$I = \frac{V}{Z_{eq}} = \frac{100 \angle 0^\circ}{6.13 \angle 14.9^\circ} = 16.31 \angle -14.9^\circ \text{ A}$$

$$I_1 = \frac{V}{Z_1} = \frac{100 \angle 0^\circ}{6.4 \angle 51.34^\circ} = 15.62 \angle -51.34^\circ \text{ A}$$


$$I_2 = \frac{V}{Z_2} = \frac{100 \angle 0^\circ}{10 \angle -53.13^\circ} = 10 \angle 53.13^\circ \text{ A}$$

* The Concept of Admittance :

Defⁿ : The admittance is defined as the reciprocal of the impedance.

It is denoted by Y & Unit is Siemens (S)

$$\therefore Y = \frac{1}{Z}$$

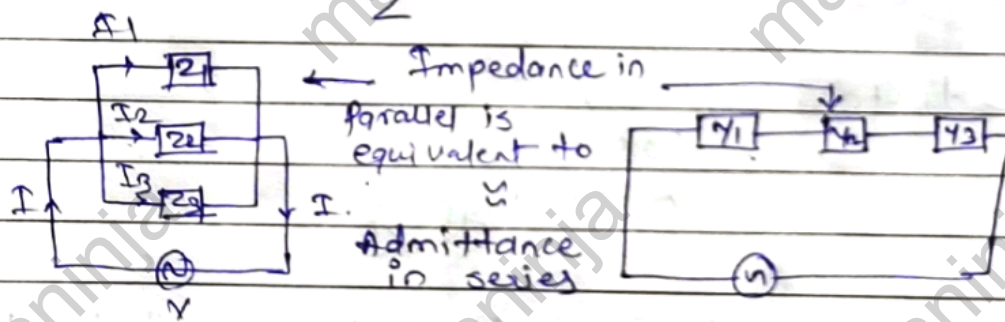

(a) Impedance in Parallel

(b) Admittance in series

$$I = I_1 + I_2 + I_3$$

Substitute the values of I_1 , I_2 & I_3 we get,

$$I = \frac{V}{Z_1} + \frac{V}{Z_2} + \frac{V}{Z_3}$$

Using Defⁿ of Admittance

$$\therefore I = VY_1 + VY_2 + VY_3$$

$$I = V(Y_1 + Y_2 + Y_3)$$

Hence the effective admittance $\bar{Y}$ is given by,

$$\therefore \bar{Y} = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3$$

* **Conductance (G) :** The Conductance (G) is defined as the ratio of the resistance (R) & the square impedance (Z^2). It is denoted by (G) & It is measured in Siemens.

$$G = \frac{R}{Z^2}$$

* **Susceptance (B) :** Susceptance (B) is defined as the ratio of the reactance $\mp X$ & the squared impedance (Z^2).

It is denoted by (B) & measured in Siemens. The Susceptance can be inductive or capacitive depending on the polarity of X.


$$\therefore B = \frac{X}{Z^2}$$

- If the polarity of susceptance is positive, it is said to be capacitive susceptance (B_C) & If the polarity is negative then the susceptance is said to be inductive susceptance (B_L).


Polarity	+	-
Reactance (X)	Inductive	Capacitive
Susceptance (B)	Capacitive	Inductive

* **Admittance Triangle :**

- For Inductive Susceptance :

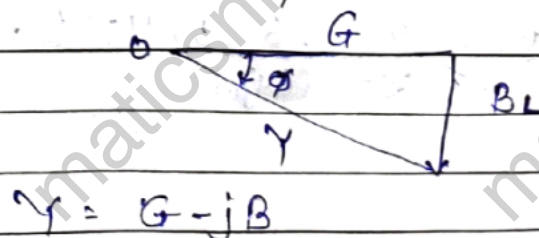

- For Capacitive Susceptance :

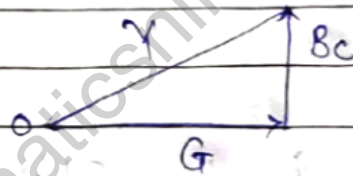

$$Y = G + jB$$

$$Y^2 = G^2 + B^2$$

$$Y = \sqrt{G^2 + B^2} \quad \tan^{-1} \left(\frac{B}{G} \right)$$

$$Y = \sqrt{G^2 + B^2}$$

* Solved Numerical by Admittance Method :

1) Calculate Conductance & Susceptance if $Z = 6 + j8 \Omega$

Soln: $Z = 6 + j8 = 10 \angle 53.13^\circ$

$$Y = \frac{1}{Z} = \frac{1}{10 \angle 53.13} = 0.1 \angle -53.13^\circ$$

In Rectangular

$$Y = 0.06 - j0.079$$

$$Y = G - jB$$

$$\text{OR Conductance (G)} = \frac{R}{Z^2} = \frac{6}{(6+j8)^2} = 0.06$$

$$\text{Sus. (B)} = \frac{X}{Z^2} = \frac{8}{(6+j8)^2} = 0.08$$

Compar with above Eqⁿ we get,

$$G = 0.06 \quad \& \quad B = -0.079$$

2) What is the value of Admittance, Conductance & Susceptance if $Z = 4 + j6$.

Soln: $Z = 4 + j6$

$$Y = \frac{1}{Z} = \frac{1}{(4+j6)} = \frac{1}{7.4 \angle 56.31} = 0.138 \angle -56.31$$

$$\text{Conductance (G)} = \frac{R}{Z^2} = \frac{4}{(4+j6)^2} = 0.076 \angle -112.61$$

$$\text{Susceptance (B)} = \frac{X}{Z^2} = \frac{6}{(4+j6)^2} = 0.115 \angle -112.61$$


3) Find Admittance of each branch, Total admittance & total current of the circuit shown in fig.

Soln:

Find: Y, Y_1, Y_2 & I

$$Z_1 = 5 + j6 = 7.81 \angle 50.19^\circ$$
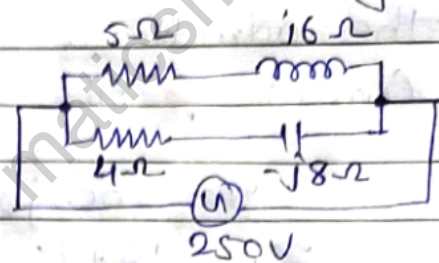
$$Z_2 = 4 - j8 = 8.94 \angle -63.43^\circ$$



$$Y_1 = \frac{1}{Z_1} = \frac{1}{7.81 \angle 50.19^\circ} = 0.128 \angle -50.19^\circ \text{ S}$$

$$= 0.081 - j0.098$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{8.94 \angle -63.43^\circ} = 0.11 \angle 63.43^\circ \text{ S}$$

$$= 0.049 + j0.098$$

$$Y = Y_1 + Y_2$$

$$= (0.081 - j0.098) + (0.049 + j0.098)$$

$$= 0.13 + j0$$

$$Y = 0.13 \angle 0^\circ \text{ S}$$

$$I = V \cdot Y$$

$$= (250 \angle 0^\circ) \cdot (0.13 \angle 0^\circ)$$


$$I = 32.5 \angle 0^\circ \text{ A}$$

4) Find the admittance of each branch find total admittance shown by circuit.

Soln:

$$Z_1 = 5 + j5 = 7.07 \angle 45^\circ$$
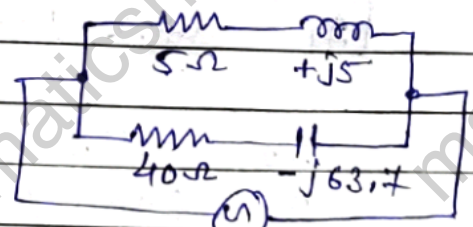
$$Z_2 = 40 - j63.7 = 75.21 \angle -57.87^\circ$$



$$Y_1 = \frac{1}{Z_1} = \frac{1}{7.07 \angle 45^\circ} = 0.141 \angle -45^\circ \text{ S}$$

$$= 0.099 - j0.099$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{75.21 \angle -57.87^\circ} = 0.013 \angle 57.87^\circ \text{ S}$$

$$= 0.006 + j0.011$$

$$Y = Y_1 + Y_2 = (0.099 - j0.099) + (0.006 + j0.011)$$

$$Y = 0.105 - j0.088 \text{ S} \quad \leftarrow \text{Ans in Rect form}$$

$$Y = 0.137 \angle -39.96^\circ \text{ S}$$

$$\leftarrow \text{Ans in Polar form}$$

5) Impedance $Z_1 = (10 + j5) \text{ ohm}$ & $Z_2 = (8 + j6) \Omega$ are connected in parallel across $V = (200 + j0)$. Using the admittance method, calculate the circuit current & the branch currents.

Soln:

$$V = 200 + j0 = 200 \angle 0^\circ$$

$$Z_1 = 10 + j5 = 11.18 \angle 26.56^\circ$$

$$Z_2 = 8 + j6 = 10 \angle 36.86^\circ$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{11.18 \angle 26.56^\circ} = 0.089 \angle -26.56^\circ = 0.08 - j0.039$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{10 \angle 36.86^\circ} = 0.1 \angle -36.86^\circ = 0.08 - j0.059$$

$$Y = Y_1 + Y_2$$

$$= (0.08 - j0.039) + (0.08 - j0.059)$$

$$Y = 0.16 - j0.098$$

$$Y = 0.18 \angle -31.48^\circ$$

$$\therefore I = V \cdot Y$$

$$= (200 \angle 0^\circ) (0.18 \angle -31.48^\circ)$$

$$\boxed{I = 36 \angle -31.48^\circ \text{ A}}$$

$$\therefore I_1 = V \cdot Y_1$$

$$I_1 = (200 \angle 0^\circ) (0.089 \angle -26.56^\circ)$$

$$\boxed{I_1 = 17.8 \angle -26.56^\circ \text{ A}}$$

$$I_2 = V \cdot Y_2$$

$$I_2 = (200 \angle 0^\circ) (0.1 \angle -36.86^\circ)$$

$$\boxed{I_2 = 20 \angle -36.86^\circ \text{ A}}$$

6) Two parallel impedances $Z_1 = (10 + j8) \Omega$ & $Z_2 = (15 - j10) \Omega$ are connected to 230V, 50 Hz AC Supply. Using admittance method, calculate branch current, total current & P.F of whole circuit.
Soln:

Given, $Z_1 = (10 + j8) \Omega$, $Z_2 = (15 - j10) \Omega$, $V = 230V$, $f = 50Hz$
Find: I_1 , I_2 , I & P.F.

Find I_1 :

$$Z_1 = 10 + j8 = 12.8 \angle 38.65^\circ \Omega$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{12.8 \angle 38.65^\circ} = 0.078 \angle -38.65^\circ S$$

$$I_1 = V \cdot Y_1 = (230 \angle 0^\circ) (0.078 \angle -38.65^\circ)$$

$$= 17.94 \angle -38.65^\circ A$$

$$I_1 = 14 - j11.20 A$$

Find I_2 :

$$Z_2 = 15 - j10 = 18 \angle -33.69^\circ \Omega$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{18 \angle -33.69^\circ} = 0.055 \angle 33.69^\circ S$$

$$I_2 = V \cdot Y_2 = (230 \angle 0^\circ) (0.055 \angle 33.69^\circ)$$

$$= 12.65 \angle 33.69^\circ A$$

$$I_2 = 10.52 + j7.01 A$$

Total Current, $I = I_1 + I_2$


$$= (14 - j11.20) + (10.52 + j7.01)$$

$$I = 24.52 - j4.19 A$$

$$= 24.87 \angle -9.69^\circ A$$

$$P.F = \cos \phi = \cos (-9.69^\circ) = 0.98 \text{ (lagging)}$$

* Resonance in Parallel RLC Circuit ?

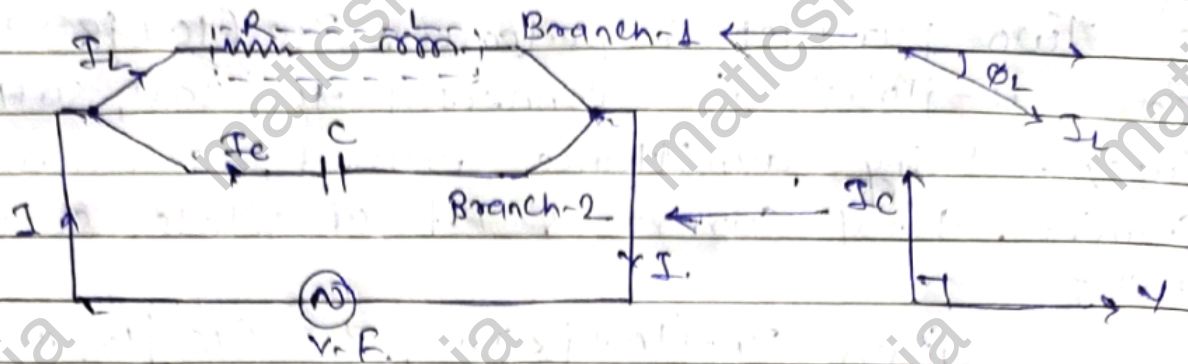


- When applied voltage (V) & total current (I) are in phase then it is called as resonance frequency of parallel ac circuit.

- In above fig. shows the two branches are connected in parallel with each other.

- First branch consist of a resistance in series with a pure inductance, whereas the other branch consists of a pure capacitor.

- Let the sinusoidal voltage V of frequency f is connect across the parallel circuit. Let the current through the first branch be I_L & that through second branch is I_C .

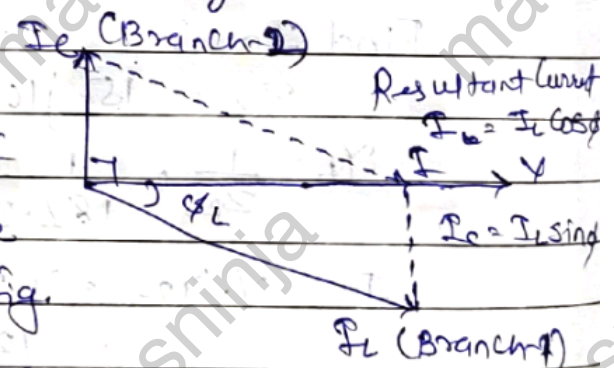- Combining the phasor diag. of individual branches we can draw the complete phasor diag. as shown in fig.



- At resonance V & I are in phase hence $\phi = 0$. Hence the power factor i.e. $\cos \phi = 1$. Therefore the resonance condition is also called as unity P.f. Condition.

$$\therefore I = I_L \cos \phi_L$$

$$I_C = I_L \sin \phi_L$$

* Expression for Resonance frequency (F_r):

- At resonance, the value of current through branch-2 is given by,

$$I_C = I_L \sin \phi_L$$

$$\text{But } I_C = \frac{V}{X_C}, \quad I_L = \frac{V}{Z_L} \quad \phi \sin \phi_L = \frac{X_L}{Z_L}$$

$$\frac{V}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L}$$

$$\frac{V}{X_C} = \frac{V \cdot X_L}{Z_L^2}$$

$$\frac{1}{X_C} = \frac{X_L}{Z_L^2}$$

$$\therefore Z_L^2 = X_L \cdot X_C$$

$$\therefore R^2 + X_L^2 = \cancel{\phi_L} \cdot \frac{1}{\cancel{\phi_C}} = \frac{1}{C} \quad \text{But } Z_L^2 = R^2 + X_L^2$$

$$X_L^2 = \frac{1}{LC} - R^2$$

$$\omega L^2 = \frac{1}{LC} - R^2$$

$$\text{But } X_L = 2\pi f L \quad \& \quad 2\pi f = \omega$$

$$\therefore X_L = \omega \cdot L$$

$$\omega^2 \cdot L^2 = \frac{1}{LC} - R^2$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$(2\pi F_r)^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$2\pi F_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$F_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

- If R is negligible we can neglect the second term in the above expression.

$$\therefore F_r = \frac{1}{2\pi \sqrt{LC}}$$

* Dynamic Impedance at Resonance (Z_D) :

The dynamic Impedance (Z_D) is defined as the impedance offered by the parallel R-L-C circuit at resonance.

• Expression for Z_D :

- The current I at resonance is given by,

$$I = I_L \cos \phi_L$$

$$\text{But } I_L = \frac{V}{Z_L} \quad \phi \cos \phi_L = \frac{R}{Z_L}$$

$$\therefore I = \frac{V}{Z_L} \times \frac{R}{Z_L}$$

$$I = \frac{V \cdot R}{Z_L^2}$$

$$\text{But } Z_L^2 = R^2 + \omega^2 L^2$$

$$I = \frac{V \cdot R}{R^2 + \omega^2 L^2}$$

$$\text{But } R^2 + \omega^2 L^2 = L/C$$

$$\therefore I = \frac{V \cdot R}{L/C}$$

$$I = \frac{V}{L/RC}$$

- The term (L/RC) is called as the dynamic Impedance.

$$\therefore \boxed{I = \frac{V}{Z_D} \quad \text{or} \quad Z_D = \frac{L}{RC}} \quad \text{or } R_D$$

Q-Factor for Parallel R-L-C circuit :

It is defined as the current magnification provided at resonance, called as Q-factor.

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Numerical on Resonance Fr, Q-Factor & Z_D

- 1) An Inductive coil having resistance of 10Ω & inductance of 0.5 H is connected in parallel with a capacitor of $50\mu\text{F}$, ^{with 230V.} Determine :


- 1) Parallel Resonance Frequency 2) Q-Factor of Parallel ckt.

Soln:

Given, $R=10\Omega$, $L=0.5\text{ H}$, $C=50\mu\text{F}$

$C=50\mu\text{F} = 50 \times 10^{-6}\text{ F}$, $V=230\text{V}$

Find: F_r & Q-Factor.

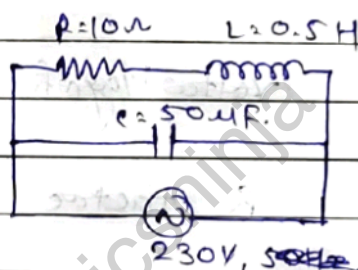

$$F_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.5 \times 50 \times 10^{-6}}} = 31.84\text{ Hz}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{0.5}{50 \times 10^{-6}}} = 10$$

- 2) A coil with $R=10\Omega$ & $L=0.25\text{ H}$ is connected in parallel with a capacitor of $100\mu\text{F}$. Find ;
Q-Factor & Dynamic Resistance.

Soln:

Given, $R=10\Omega$, $L=0.25\text{ H}$ & $C=100\mu\text{F} = 100 \times 10^{-6}\text{ F}$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{0.25}{100 \times 10^{-6}}} = 5$$

$$R_D = \frac{L}{RC} = \frac{0.25}{10 \times 100 \times 10^{-6}} = 250\Omega$$

* Comparison of Series & Parallel Resonant Ckt :

Sr. No.	Parameter	Series Ckt	Parallel Ckt
1)	Impedance	Min. $Z = R$	Max. $Z_D = L/CR$
2)	Nature of Circuit	Resistive	Resistive
3)	Power Factor	Unity (1)	Unity (1)
4)	Current Drawn from the Source	Max. $I = \frac{V}{Z}$	Min. $I = \frac{V}{(L/CR)}$
5)	Resonance frequency	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi\sqrt{LC}}$
6)	Voltage Magnification	Voltage Magn. takes Place	Current magn. takes Place
7)	Q-factor	$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$	$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$
8)	Application	As an acceptor ckt	As a rejector ckt.

[Signature]

Subject T/C
Mr. BhosiWale G.H