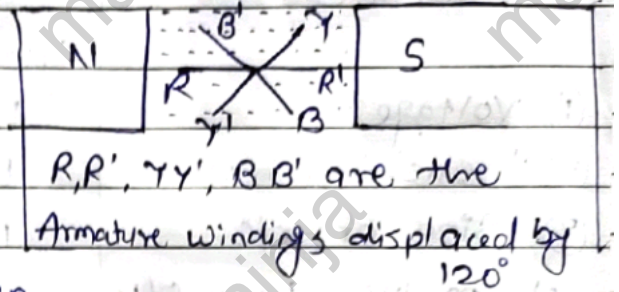


## Unit - 3 Three Phase Circuits

### \* Generation of 3 phase alternating EMF :

#### • Principle :

- The single phase supply is generated using a single turn alternator. Thus if armature consists of only one winding, then only one alternating voltage is produced.



- But if the armature winding is divided into three groups which are displaced by  $120^\circ$  from each other, then it is possible to generate three alternating vtg.

#### • Construction :


- As shown in above fig. the armature winding is divided into three groups. The three coils are  $R-R', Y-Y' \& B-B'$ .

- All these coils are mounted on the same shaft & are physically placed at  $120^\circ$  from each other.

- When these coils rotate in the flux produced by the permanent magnet, emf is induced into these coils.
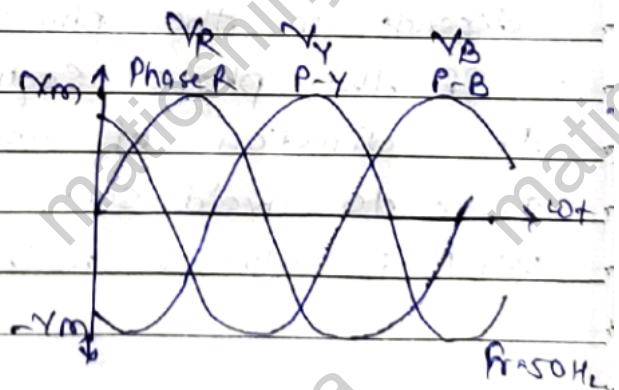
#### • Waveforms :

- These emf as shown in fig. are sinusoidal of equal amplitude & equal frequency but they are displaced by  $120^\circ$  from each other.



-  $V_R, V_Y \& V_B$  are 3-ph vtg. If fig. vtg induced in 3 coil  $V_R$  is considered as reference, then  $V_Y$  lags  $V_R$  by  $120^\circ$  &  $V_B$  lags  $V_Y$  by  $120^\circ$ .

## \* Comparison of 1-ph & 3-ph System :

| Parameter                           | 1-ph System                       | 3-ph System                         |
|-------------------------------------|-----------------------------------|-------------------------------------|
| ① Voltage                           | Low (230V)                        | High (415V)                         |
| ② Transmission $\eta$               | Low                               | High                                |
| ③ Size of m/c to produce same o/p   | Larger                            | Smaller                             |
| ④ Cross sectional area of conductor | Larger                            | Small                               |
| ⑤ Application                       | Domestic, Small power application | Industrial, large power application |

## \* Phase Sequence :

• Definition - The phase sequence is defined as the sequence in which the three phases reach their maximum positive values. Normally the phase sequence is R-Y-B. The three phase colours used to denote 3 ph's are Red, Yellow & Blue.

### • Importance of Phase Sequence :

- The direction of rotation of the three phases machine depends on the phase sequence.
- If the phase sequence is changed e.g. R-B-Y then the direction of rotation will be reversed. In order to avoid such things, the phase sequence of R-Y-B is always maintained.



## \* Types of Three Phase Connection :

1> Star Connection

2> Delta Connection

1> Star Connection (Wye Connection) :

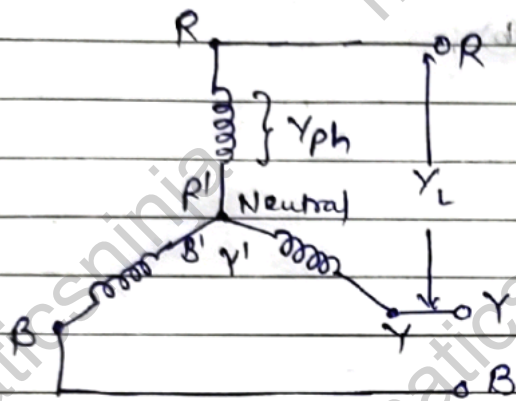


fig. (a) Star Connection

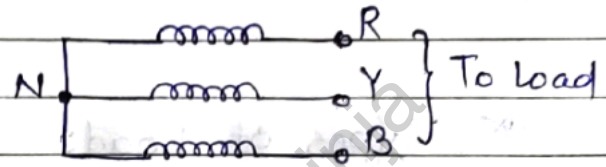


fig. (b) Equivalent circuit

- In above fig. Shows the Star or Wye Connection of the three alternator winding.
- This configuration is obtained by connecting one end of the three phase winding together.
- We can connect either R, Y, B or R', Y', B' together. This common point is called as the Neutral Point & It is denoted by N.
- The three remaining end of the winding are brought out for the external connection. These ends are denoted by R-Y-B as shown in fig. (b).

2> Delta Connection :

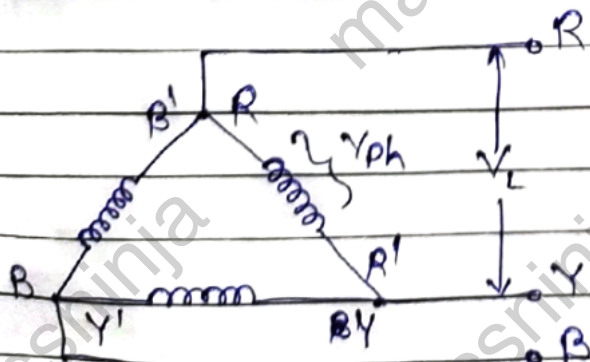


fig. (a) Delta or Mesh Connection

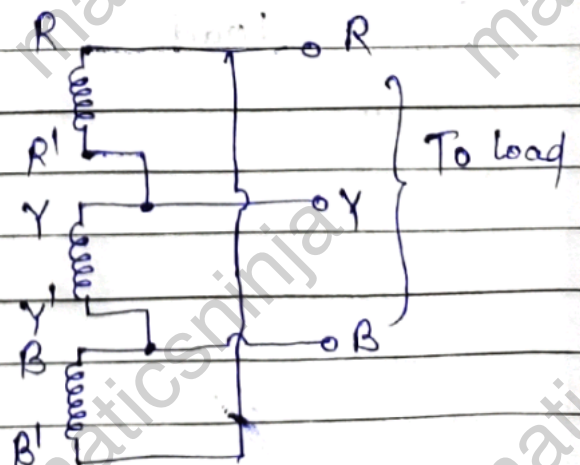


fig. (b) Equivalent circuit

- In above fig. Shows the delta Connection or mesh Conn. of the three alternator winding.
- In delta or mesh configuration is obtained by connection one end of winding to the starting end of the other winding such that it produces a closed loop as shown in fig. (b).

### \* Types of Loads :

- 1) Balanced Load
- 2) Unbalanced Load

#### 1) Balanced Load :

Defn : A balanced load is that in which magnitude of all impedances connected in the load are equal & the phase angles of them also are equal it is called as balanced load.

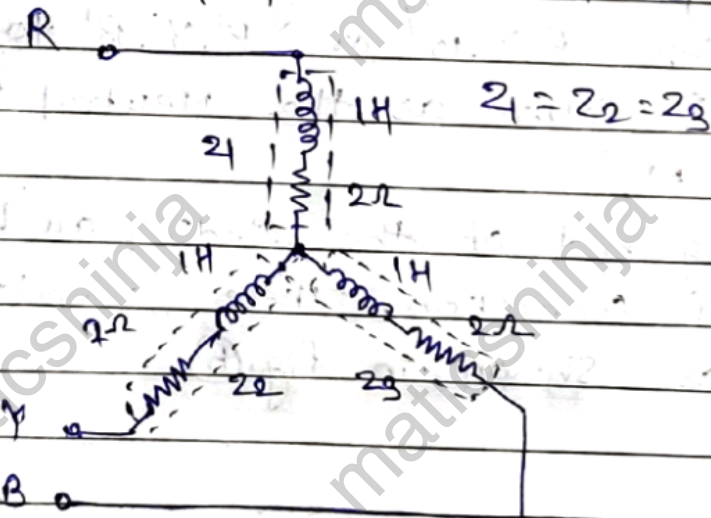


fig. (a) Balanced Star Connected Load.

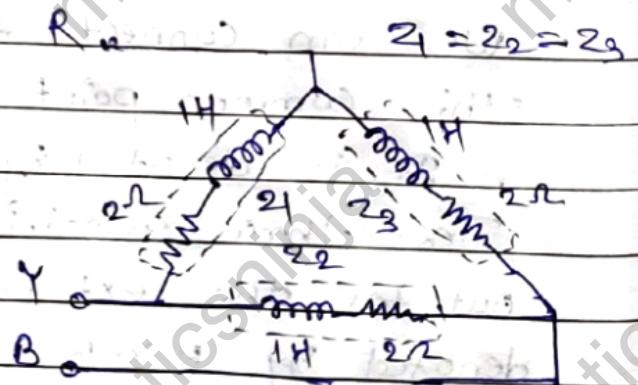


fig. (b) Balanced Delta Connected Load.



## 2) Unbalanced Load :

- Def<sup>n</sup> : If a load does not satisfy the condition of balanced, then it's called as the Unbalanced load.
- If the magnitude & phase angle of the three impedances  $Z_1$ ,  $Z_2$  &  $Z_3$  diff. from each other, then the load is said to be unbalanced.

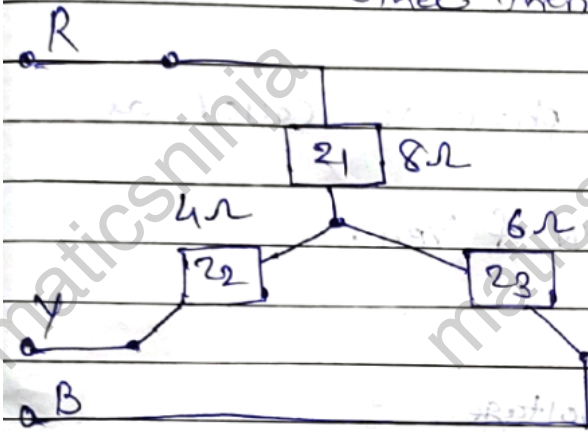


fig. (a) Unbalanced Star load

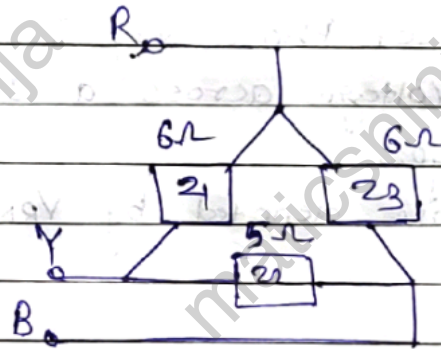


fig. (b) Unbalanced delta load

- In fig. (b)  $Z_1 = Z_3 = 6\Omega$  still this is an unbalanced delta connection because all the impedances are not equal.

## \* Three Phase Balanced Star Load :

- Line Voltage & Phase Voltage for Star Connected Supply :

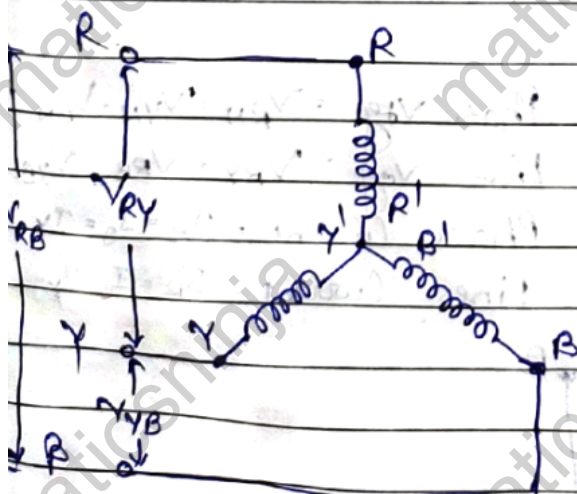


fig. (a) Line voltage

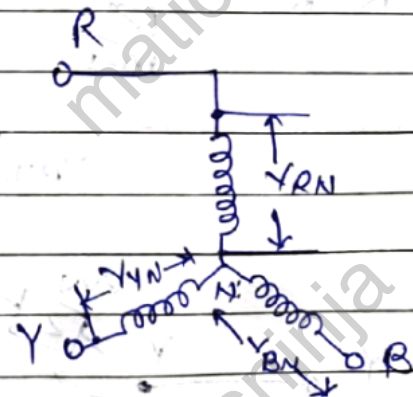


fig. (b) Phase voltage

## • Definition of line v<sub>tg</sub> :

- If R, Y & B are called as supply lines, then the potential difference bet<sup>n</sup> any two lines is known as the line v<sub>tg</sub>.
- $V_{RY}$ ,  $V_{RB}$ ,  $V_{YB}$ ,  $V_{YR}$ ,  $V_{BR}$  &  $V_{BY}$  are six possible line voltages.

## • Definition of Phase v<sub>tg</sub> :

- The voltage across a single phase is called as phase voltage.
- They are denoted by  $V_{RN}$ ,  $V_{YN}$  &  $V_{BN}$ .


## \* Relation bet<sup>n</sup> Phase & Line Voltage :

- For a star connected load, the magnitude of line v<sub>tg</sub> is  $\sqrt{3}$  times higher than that of a phase v<sub>tg</sub>.

$$\therefore \boxed{V_L = \sqrt{3} V_{ph}}$$

## \* Relation bet<sup>n</sup> Phase & Line Current :
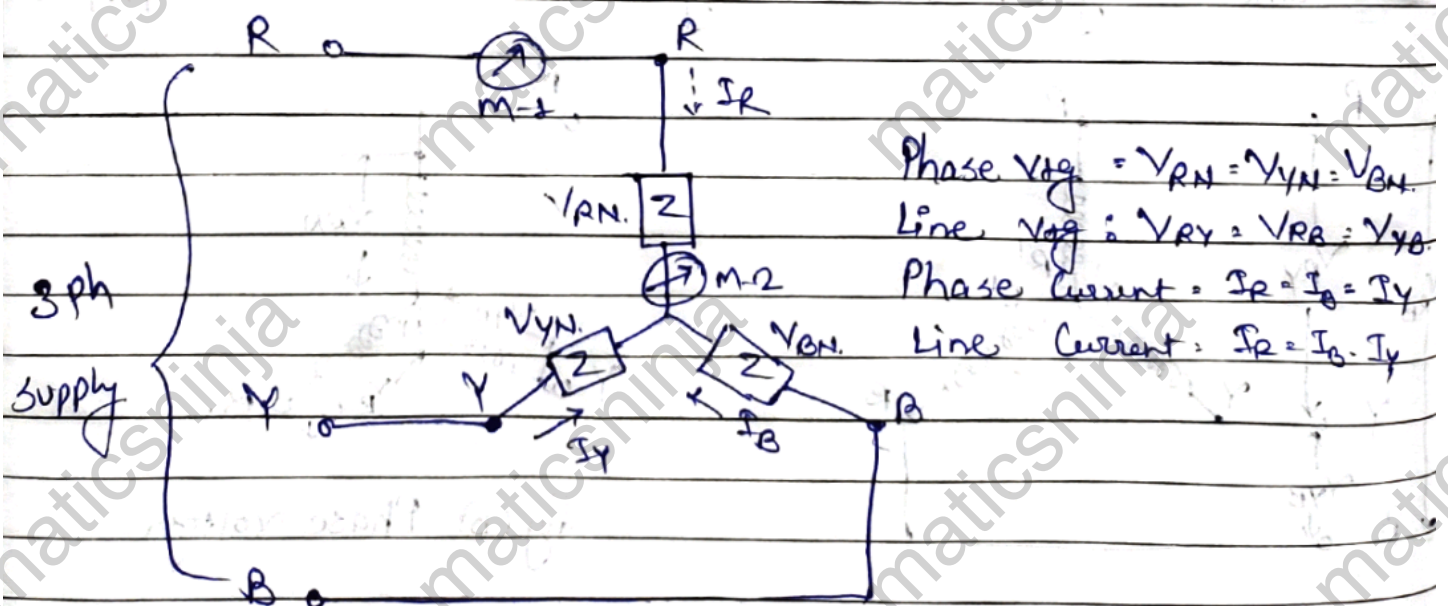
### \* Line & Phase Current for star connected supply :





### • Definition of Phase Current :

- The current passing through any branch of the star connected load is called as phase current.
- $I_R, I_Y$  &  $I_B$  are the phase currents.
- Meter - 2 measures the phase current  $I_R$ .

### • Definition of Line Current :

- The current passing through any line R, Y, B is called as line current.
- Meter - 1 measured the line current.
- It is denoted by  $I_L$ .


### • Relation betn Phase & Line Current :

- As the current flowing through each branch line is equal to the current flowing through the corresponding branch, the line current is equal to the phase current.

$$\therefore \boxed{I_L = I_{ph}}$$

### \* The Complete Phasor diagram :

(Line vlg)

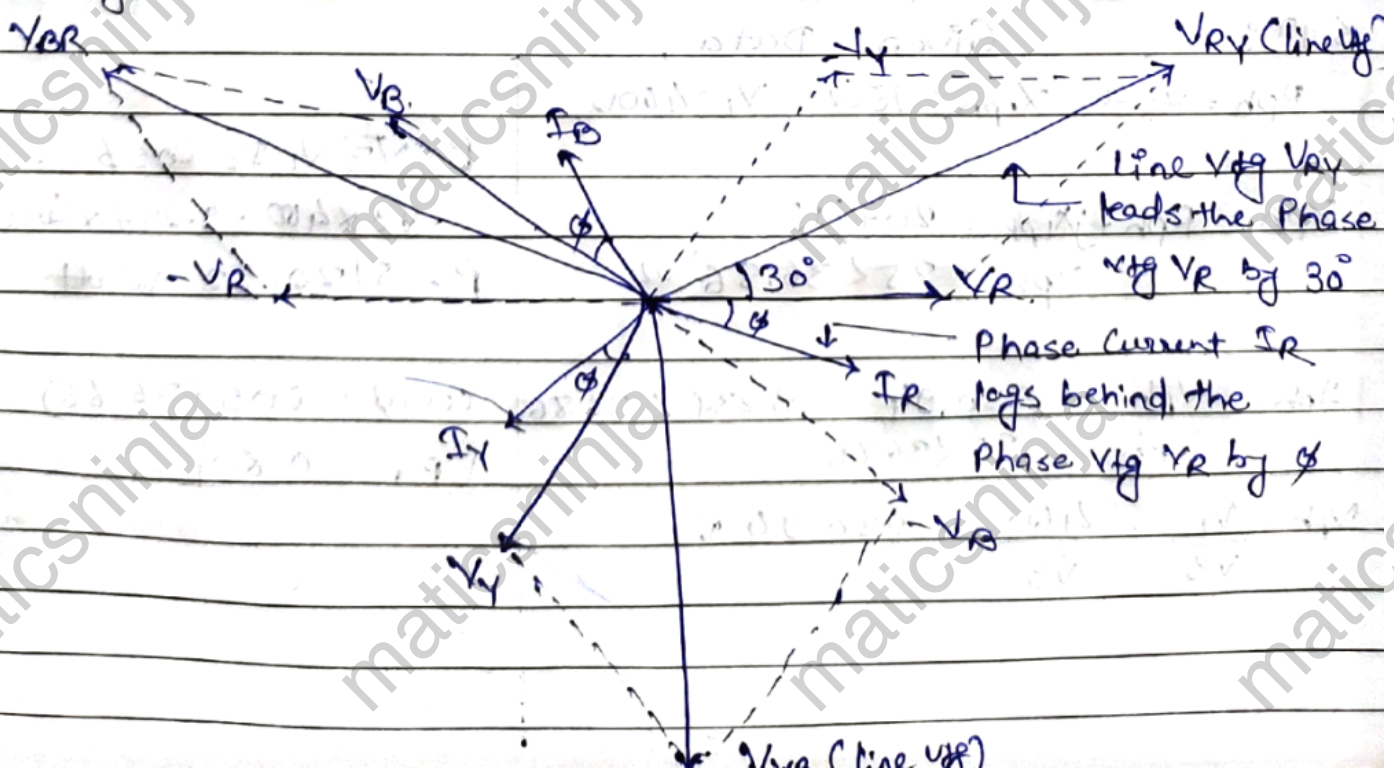

## Numerical on Star Load :

- ① A 3-ph Star Connected load has a resistance of  $16\Omega$  & an inductive reactance of  $12\Omega$  in each branch. It is supplied from 3 ph  $400V$ ,  $50Hz$  supply. Calculate line & Phase current & Power input in Watt.

Sol<sup>n</sup>: Given Data,

$$R_{ph} = 16\Omega, X_{Lph} = 12\Omega, f = 50Hz, V_L = 400V,$$

$$\text{In star } I_L = I_{ph}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{20 \angle 36.86^\circ} = 11.547 \angle -36.86^\circ A$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94 V$$

$$Z_{ph} = R_{ph} + jX_{Lph} = 16 + j12 = 20 \angle 36.86^\circ$$

$$I_L = I_{ph} = 11.547 \angle -36.86^\circ A \quad \dots \text{Ans}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$P = \sqrt{3} \times 400 \times 11.547 \times \cos(-36.86^\circ)$$

$$P = 6400.82 \text{ Watt} \quad \dots \text{Ans}$$

- ② Three coil each having a resistance of  $20\Omega$  & reactance of  $15\Omega$  are connected in star to a  $400V$ ,  $3ph$ ,  $50Hz$  supply. Calculate: ① Line current ② Power supplied ③ Power factor.

Sol<sup>n</sup>: Given Data,

$$R_{ph} = 20\Omega, X_{Lph} = 15\Omega, V_L = 400V,$$

$$Z_{ph} = R_{ph} + jX_{Lph} = 20 + j15$$

$$Z_{ph} = 25 \angle 36.86^\circ \Omega$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{25 \angle 36.86^\circ} = 9.237 \angle -36.86^\circ$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94 V$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 9.237 \times \cos(36.86^\circ)$$

$$P = 5120.32 \text{ Watt}$$

$$\cos \phi = \cos(36.86^\circ)$$

$$\boxed{P.F. = 0.80}$$



③ Three coil each with a resistance of  $10\Omega$  & inductance of  $0.35\text{ mH}$  are connected in star to a 3ph-400V, 50Hz supply. Calculate line current & total power consumed.

Soln: Given Data, Star Load.

$$R_{ph} = 10\Omega, L = 0.35\text{ mH}, V_L = 400\text{ V}, f = 50\text{ Hz}$$

Find:  $I_L$  &  $P$

$$X_{Lph} = 2\pi f L_{ph} = 2 \times 3.14 \times 50 \times 0.35 = 109.9\Omega$$

$$Z_{ph} = \sqrt{(R)^2 + (X_L)^2} = \sqrt{(10)^2 + (109.9)^2} = 110.35 \angle 84.8^\circ$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94\text{ V}$$

$$\therefore I_{ph} = I_L = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{110.35 \angle 84.8^\circ} = 2.09 \angle -84.8^\circ\text{ A}$$


$$P = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 2.09 \times \cos(84.8^\circ)$$

$$P = 131.23\text{ Watt}$$
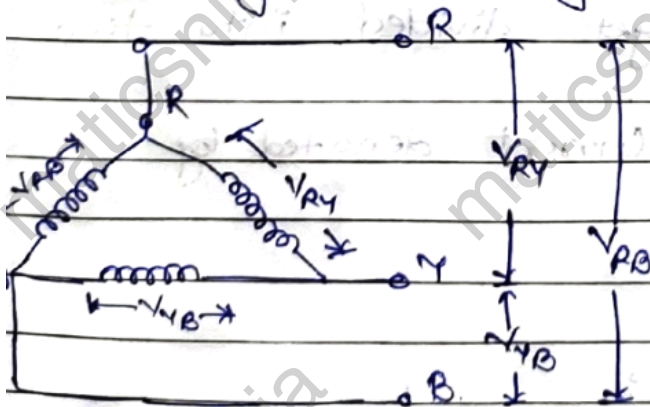
### \* Three Phase Balanced Delta Load :

• Line  $V_{tg}$  & Phase  $V_{tg}$  for Delta Connected Supply :



• Line  $V_{tg}$  : The line  $V_{tg}$  is defined as the potential diff. betn two line. So  $V_{RY}$ ,  $V_{YB}$  &  $V_{BR}$  are the line  $V_{tg}$ .

• Phase  $V_{tg}$  : The  $V_{tg}$  measured across a single winding is called as the  $V_{tg}$  phase  $V_{tg}$ .

Fig. Delta Connection

• Note that  $V_{RY}$ ,  $V_{YB}$  &  $V_{BR}$  which are same as line  $V_{tg}$ . Thus for delta connected supply, the phase  $V_{tg}$  are same as line  $V_{tg}$ .


\* Relation betn Phase & Line Vtg :

- for delta connected supply the phase Vtg  $V_{RY}$ ,  $V_{YB}$  &  $V_{BR}$  are ~~same~~ and line voltage also  $V_{RY}$ ,  $V_{YB}$  &  $V_{BR}$ .

$$\therefore V_{ph} = V_L = V_{RY}, V_{YB}, V_{BR}$$

$$\boxed{V_{ph} = V_L}$$

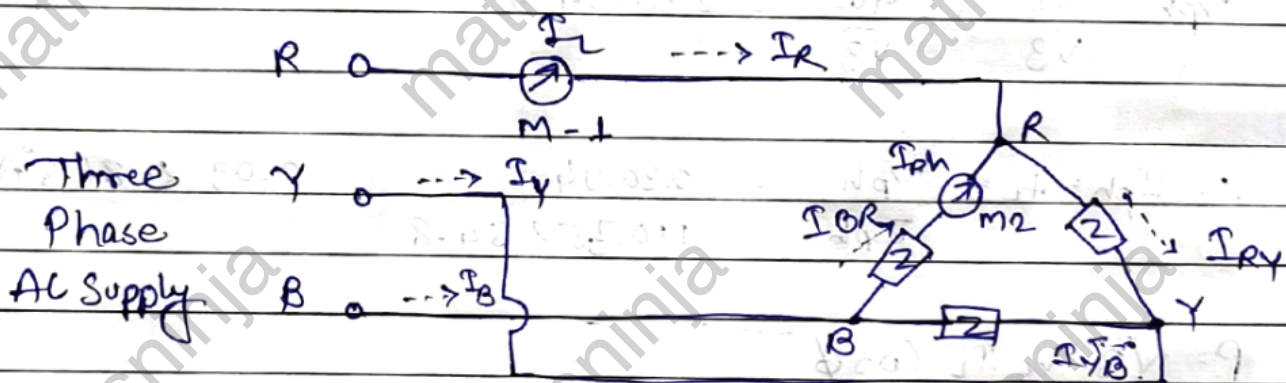\* Line & Phase Current for Delta Connection :



Phase Currents  $I_{RY}$ ,  $I_{YB}$ ,  $I_{BR}$   
Line Currents  $I_R$ ,  $I_Y$ ,  $I_B$

- Line Current : It is denoted by  $I_R$ ,  $I_Y$  &  $I_B$
- ~~Phase Current~~ : - The line current is higher than the phase current. This is because at node R, the line current  $I_R$  gets divided into two phase current  $I_{RY}$  &  $I_{BR}$ .
- So that the phase current denoted by  $I_{RY}$ ,  $I_{YB}$ , &  $I_{BR}$ .


\* Relation betn  $I_L$  &  $I_{ph}$  :

- The relation betn line current & Phase current for a delta connected balanced load is as follow :

$$\boxed{I_L = \sqrt{3} I_{ph}}$$



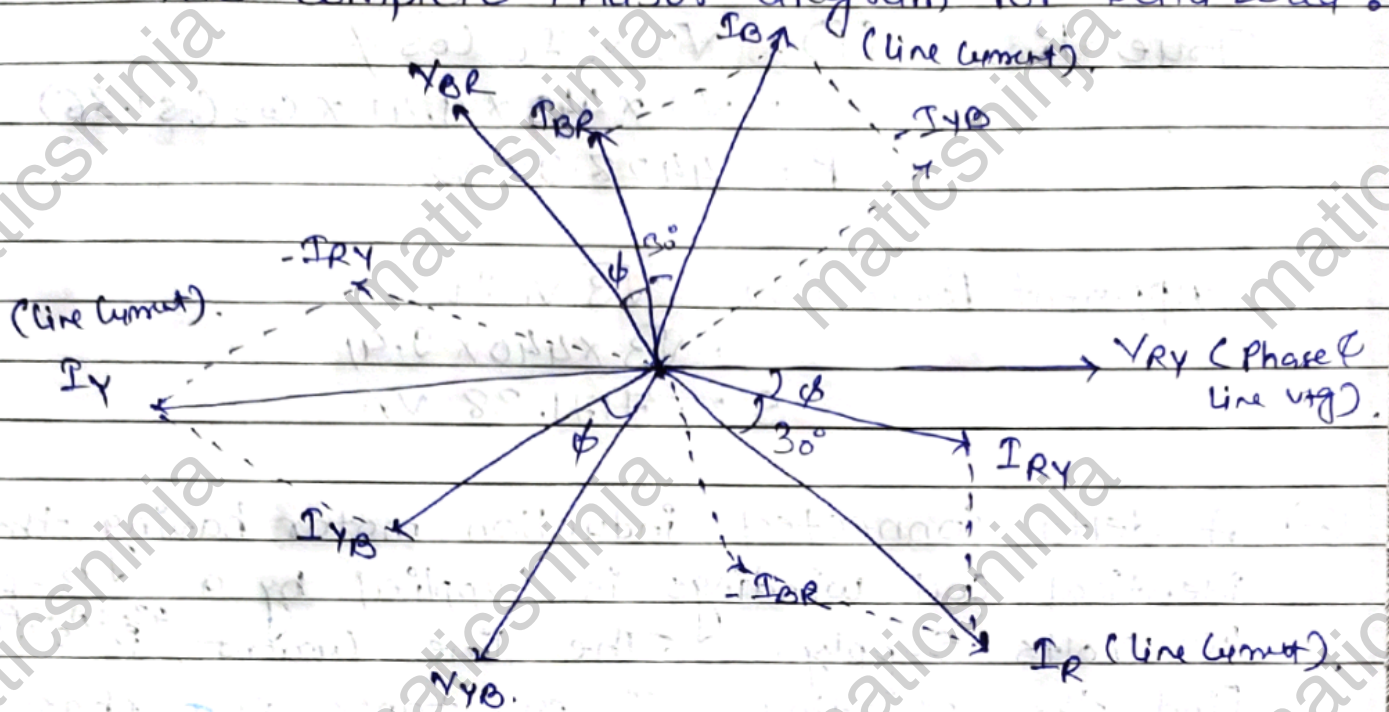\* The Complete Phasor diagram for Delta Load :



\* Numerical on Delta Connected Load (Balanced) :

- ① A Three-phase delta connected balanced load having a resistance of  $50 \Omega$  / Phase & Capacitance of  $50 \mu F$  / Phase, is supplied by  $440V, 3\phi, 50Hz$  AC Supply. Determine : ① Line Current ② Phase Current ③ True Power ④ Apparent P/W.

Soln: Given Data,

$$R = 50 \Omega / \text{ph}, C = 50 \mu F / \text{Phase}, V_L = V_{ph} = 440V, 3\phi, f = 50Hz.$$

$$I_L = \sqrt{3} I_{ph} = \sqrt{3} \times 4.94 = 8.54 A$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{440}{89.97} = 4.94 A$$

$$Z_{ph} = \sqrt{R^2 + X_c^2} = \sqrt{(50)^2 + (63.69)^2} = 80.97 \angle 51.86^\circ \Omega$$

$$X_c = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 50 \times 10^{-6}} = 63.69 \Omega$$

$$\begin{aligned}\text{True Power (P)} &= \sqrt{3} V_L I_L \cos \phi \\ &= \sqrt{3} \times 440 \times 9.41 \times \cos(51.86^\circ) \\ P &= 4428.93 \text{ W}\end{aligned}$$

$$\begin{aligned}\text{Apparent Power (S)} &= \sqrt{3} V_L I_L \\ &= \sqrt{3} \times 440 \times 9.41 \\ S &= 7171.38 \text{ VA}\end{aligned}$$

② A delta connected induction motor having three identical coil windings is supplied by a 3-ph 400 Volts supply. The line current is 43.3 A. Power is 24 kW. Find the resistance & reactance per phase of the winding.

sol<sup>n</sup>: Given Data,

$$I_L = 43.3 \text{ A}, P = 24 \text{ kW}, V_L = 400 \text{ V}$$

$$\text{for delta connection, } V_L = V_{ph} = 400 \text{ V}$$

$$I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{43.3}{\sqrt{3}} = 25 \text{ A}$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{400}{25} = 16 \Omega$$

$$\begin{aligned}P &= \sqrt{3} V_L I_L \cos \phi \\ 24 \times 10^3 &= \sqrt{3} \times 400 \times 43.3 \times \cos \phi \\ \cos \phi &= \frac{24 \times 10^3}{\sqrt{3} \times 400 \times 43.3} = 0.8\end{aligned}$$

$$\cos \phi = \frac{R_{ph}}{Z_{ph}}$$

$$R_{ph} = Z_{ph} \cos \phi = 16 \times 0.8 = 12.8 \Omega$$

$$\sin \phi = \frac{X_{ph}}{Z_{ph}}$$

$$X_{ph} = Z_{ph} \sin \phi = 16 \times \sin(36.86^\circ) = 9.59 \Omega$$



③ A delta connected load having phase impedance of  $(8+j6)\Omega$  supplied by a star connected alternator, having line voltage of 230V. Determine:

- ① Phase Current ② Line Current ③ Power factor ④ R.P.G. (8)

Soln: Given Data,

$$Z_{ph} = (8+j6)\Omega, \quad V_L = V_{ph} = 230V$$

$$Z_{ph} = \sqrt{R^2 + X^2} = \sqrt{8^2 + 6^2} = 10\Omega$$

$$P.f = \cos\phi = \frac{R}{Z_{ph}} = \frac{8}{10} = 0.8$$

$$\sin\phi = \frac{X}{Z} = \frac{6}{10} = 0.6$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230}{10} = 23A$$

$$I_L = \sqrt{3} \times I_{ph} = \sqrt{3} \times 23 = 39.83A$$

$$\begin{aligned} \text{Reactive Power (Q)} &= \sqrt{3} V_L I_L \sin\phi \\ &= \sqrt{3} \times 230 \times 39.83 \times 0.6 \\ &= 9522VA = 9.522KVA \end{aligned}$$

④ A three phase system supplied a load of 30kW at a P.f of 0.8. The line v<sub>tg</sub> is 250V. If the load is connected in ① star ② Delta, then Calculate Line Current & Phase Current.

Soln: Given Data,

$$P = 30KW, \quad P.f = \cos\phi = 0.8, \quad V_L = 250V.$$

• For star connected load:

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{250}{\sqrt{3}} = 144.33V$$

$$P = \sqrt{3} V_L I_L \cos\phi$$

$$I_L = \frac{30 \times 10^3}{\sqrt{3} \times V_L (250) \times 0.8} = 86.6A$$

$$I_L = I_{ph} = 86.6A$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{144.33}{86.6} = 1.66 \Omega$$



• For Delta Connected Load :

$$V_L = V_{ph} = 250 \text{ V.}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{250}{1.66} = 150.6 \text{ A.}$$

$$I_L = \sqrt{3} I_{ph} = \sqrt{3} \times 150.6 = 260.84 \text{ A.}$$

\* Comparison of Star & Delta Connection :
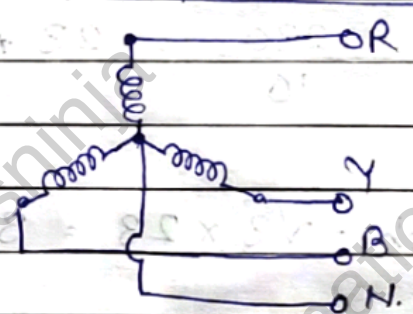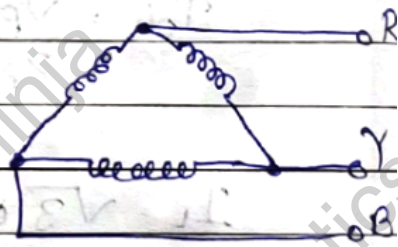
| Sr. No. Parameter      | Star Connection                                                                     | Delta Connection                                                                     |
|------------------------|-------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------|
| ① Way of Connection    |  |  |
| ② Voltage Relationship | $V_L = \sqrt{3} V_{ph}$                                                             | $V_L = V_{ph}$                                                                       |
| ③ Current Relationship | $I_L = I_{ph}$<br>$I_{ph} = V_{ph}/Z_{ph}$                                          | $I_L = \sqrt{3} I_{ph}$                                                              |
| ④ Neutral wire         | Can be Connected                                                                    | Not necessary                                                                        |

*[Signature]*

Subject T/C

Mr. Bhosiwale, G.H